

INF 5460
**Electronic noise – estimates and
countermeasures**

Lecture 4
Grounding (Ott3)

3 Grounding (Ott 3)

- 3.1 AC power distribution and safety grounds
- 3.2 Signal grounds
- 3.3 Equipment grounding
- 3.4 Ground loops
- 3.5 Low-frequency analysis of common-mode choke
- 3.6 High-frequency analysis of common-mode choke
- 3.7 Single ground reference for a circuit

Types of grounding

- Two kinds of grounding:
 - Power ground (heavy current/security ground)
 - Signal ground

3.1 AC POWER DISTRIBUTION AND SAFETY GROUNDS

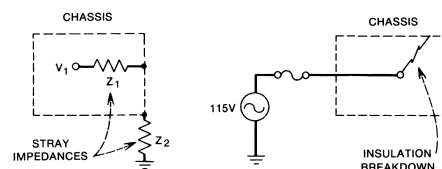


Figure 3-1. Chassis should be grounded for safety. Otherwise, it may reach a dangerous voltage level through stray impedances (left) or insulation breakdown (right).

Assume the chassis is not grounded ($Z_2 \gg 0\Omega$):

V_1 is an internal point at a high voltage connected to the high voltage mains. The voltage potential on the chassis can be expressed as:

$$V_{chassis} = \left(\frac{Z_2}{Z_1 + Z_2} \right) V_1$$

Typically Z_1 and Z_2 are both large while the ratio between them may be arbitrary. That means that the voltage on the chassis may be close to V_1 . If an electrically grounded person is touching the chassis he/she may experience an unpleasant electrical shock even though the current is small (small current due to large Z_1).


The right side of figur 3-1 shows a more dangerous situation. The figure illustrates an example where the isolation is broken so that Z_1 is close to 0Ω . Hence the chassis may have a voltage of V_1 . The chassis may deliver a maximum current decided by the fuse. If an electrically grounded person touches the chassis the entire current may pass through his/her body with fatal consequences.

If, on the other hand the chassis was grounded

- The current would pass through the ground cable instead of the person.
- The cable would be low ohmic resulting in a high current making the fuse go within short time with the result that the chassis lose the voltage.

Mains power systems:

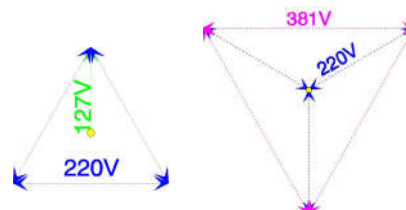- Norwegian (220V/310V)
- American (115V/220V)



(Old) Norwegian system:

The traditional Norwegian system has three phases with 120 degrees between the phases. Ground is in the middle and not used for anything else than security. Loads are connected between pairs of the phases (3 combinations). 220Vrms between two phases (Approx. 127Vrms between all phases and ground.)

Colours: Yellow or Yellow/Green for ground. Black, white and blue for the three phases. Brown and sometimes blue after a switch. Red is not common and should not be used.

New Norwegian system:

The voltage between ground and the three phases are increased to 220V for standard use. The voltage between the phases (381V) are used for more power hungry equipment. This system are used in larger buildings.

American system:

Ground used both for security ground and as fixed current return but in two different cables. Supply phase 115V from ground.

115V system:

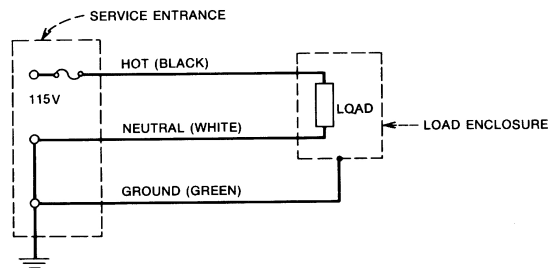


Figure 3-2. Standard 115-V ac power distribution circuit has three leads.

Fuse only on the 115V phase. Ground for return current and security ground connected in local trafo station.

230V system:


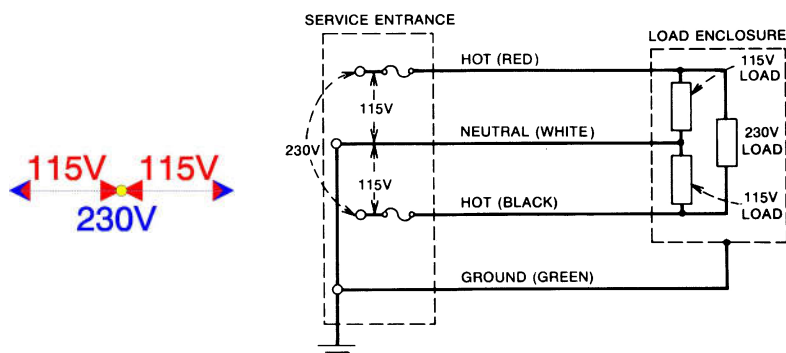



Figure 3-3. Combination 115/230-V ac power distribution circuit has four leads.

3.2 SIGNAL GROUND

A low impedance path for return current.

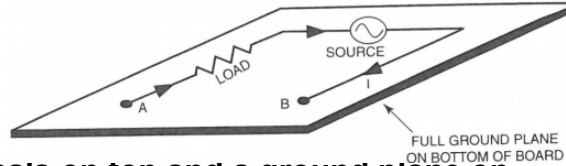

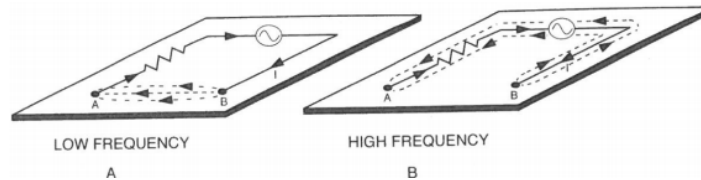A two plane board with signals on top and a ground plane on the bottom plane. At low frequencies the current follows the shortest path while at high frequencies it follows close to the signal path



Single and multipoint ground

(A low impedance path for return current.)

Three alternative architectures:

1) One point ground, 2) Multi point ground, 3) Hybrid ground

1. One point ground

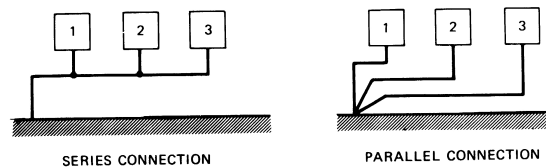


Figure 3-4. Two types of single-point grounding connections.

The serial routing is the most common but also the most noisy.

2. Multi point ground

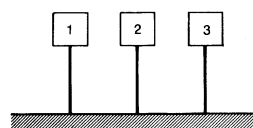


Figure 3-5. Multipoint grounding connections.

One point ground - serial

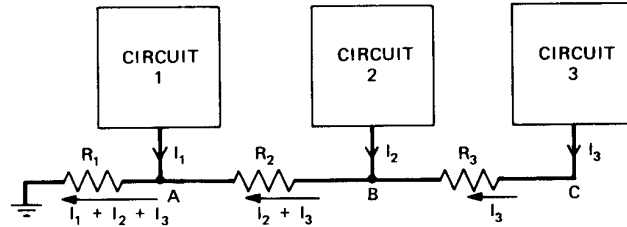


Figure 3-6. Common ground system is a series ground connection and is undesirable from a noise standpoint but has the advantage of simple wiring.

$$V_A = (I_1 + I_2 + I_3)R_1$$

$$V_C = (I_1 + I_2 + I_3)R_1 + (I_2 + I_3)R_2 + I_3R_3$$

Single line with significant common noise.

One point ground - parallel

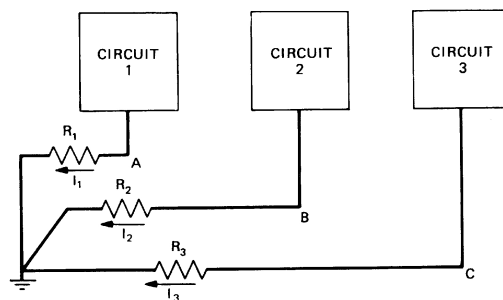


Figure 3-7. Separate ground system is a parallel ground connection and provides good low-frequency grounding but is mechanically cumbersome.

$$V_A = I_1R_1$$

$$V_C = I_3R_3$$

Less noise but more wiring.

Not suitable for longer lines and higher frequencies. $L \ll \lambda/20$.

Multi point ground

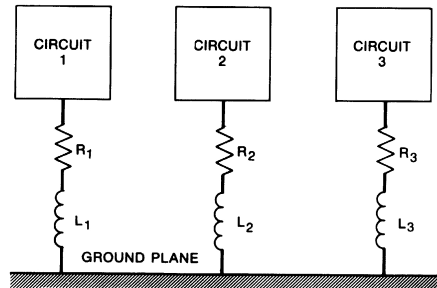


Figure 3-8. Multipoint ground system is a good choice at frequencies above 10 MHz. Impedances R_1 – R_3 and L_1 – L_3 should be minimized.

Used for higher frequencies ($>10\text{MHz}$) and in digital designs when it is important to reduce the inductance because ωL may be significant. At lower frequencies when the resistance (say in the ground plane) is more essential than the inductance, this solution should not be used. Instead an one point parallel solution should be selected.

Hybrid ground (#1/2)

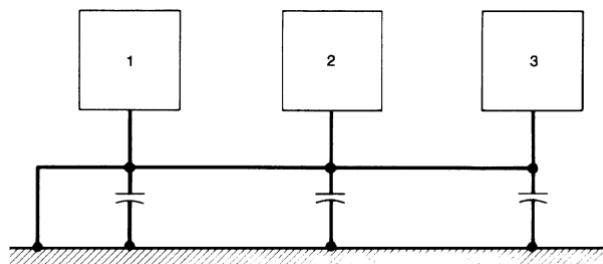


Figure 3-9. A hybrid ground connection that acts as a single-point ground at low frequencies and a multipoint ground at high frequencies.

Fig. 3.9: Behave as a one point ground at lower frequencies and a multipoint ground at higher frequencies. Used to ground cables and/or shields.

Hybrid ground (#2/2)

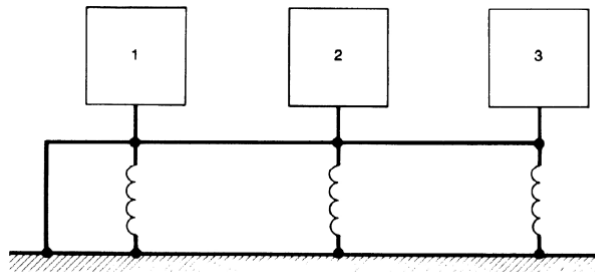


Figure 3-10. A hybrid ground connection that acts as a multipoint ground at low frequencies and a single-point ground at high frequencies.

Fig. 3.10: Multi point grounding at lower frequencies and one point grounding at higher frequencies. Used, say, when a low frequency coupling to the security ground for the mains is needed for each module at the same time as we want a single point grounding at the higher frequencies.

3.3 EQUIPMENT GROUNDING

Example 1:

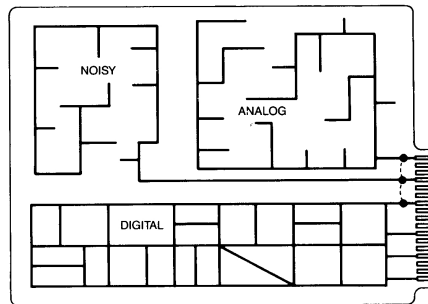


Figure 3-11. A printed wiring board with three separate ground systems, one for the digital logic, one for the low-level analog circuits, and one for the “noisy” circuits.

Here we have separated routing to avoid common impedance. Multi point grounding for the digital part, one point serially for the “noisy” part and one point parallel for the “analogue” part.

The chosen layout is a compromise between

- Design for low noise requiring more space and
- Design accepting more noise and requiring less space.

An example of a common grounding strategy is one line for each of three classes:

- Noise sensitive modules
- Noise generating modules
- Cabinet, chassis

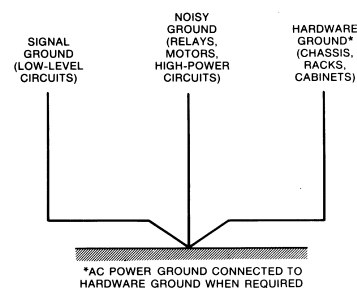


Figure 3-12. These three classes of grounding connections should be kept separate to avoid noise coupling.

Example 2:

The common connection point for the ground lines should be as close as possible to the power supply.

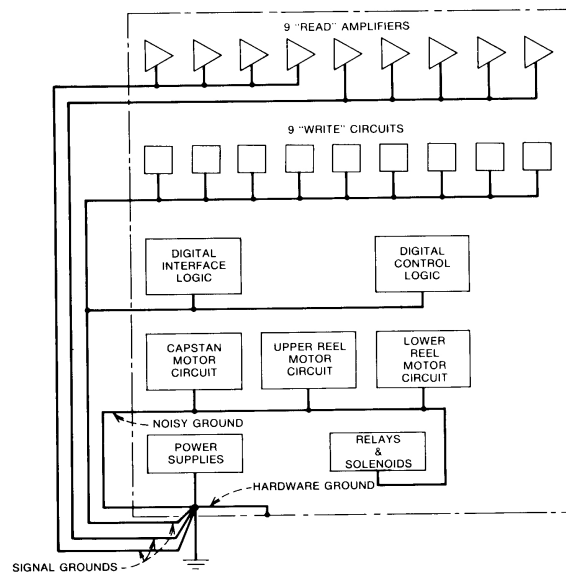


Figure 3-13. Typical grounding system for nine-track digital tape recorder.

Example 3

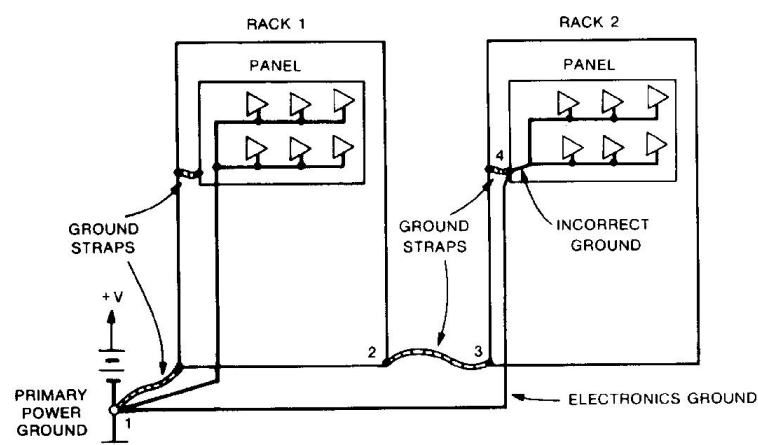


Figure 3-14. Electronic circuits mounted in equipment racks should have separate ground connections. Rack 1 shows correct grounding; rack 2 shows incorrect grounding.

One contra two points grounding of a sensor- amplifier system.

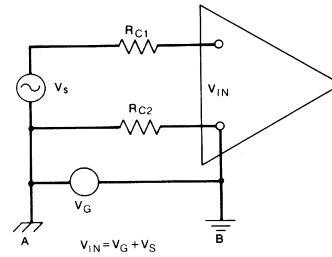


Figure 3-15. Noise voltage V_G will couple into the amplifier if the circuit is grounded at more than one point.

V_S is the wanted source signal.

V_G is the unwanted voltage difference between the two ground points. A and B is both ground points that is connected together and that ideally should have the same potential. However for different possible reasons there is a minor difference in potential between these two ground points. This is illustrated by using different ground symbols for the two points.

Alternative 1: Two ground connections

When

$$R_{C2} \ll R_S + R_{C1} + R_L$$

we have that

$$V_N = \left[\frac{R_L}{R_L + R_{C1} + R_S} \right] \left[\frac{R_{C2}}{R_{C2} + R_G} \right] V_G$$

Example:

$$V_G = 10A \cdot 0.01\Omega = 100mV$$

V_G may be due to magnetic coupling or due to passing currents running in ground.

$$R_S = 500\Omega,$$

$$R_{C1} = R_{C2} = 1\Omega,$$

$$R_L = 10k\Omega,$$

$$\Rightarrow V_N = 95mV.$$

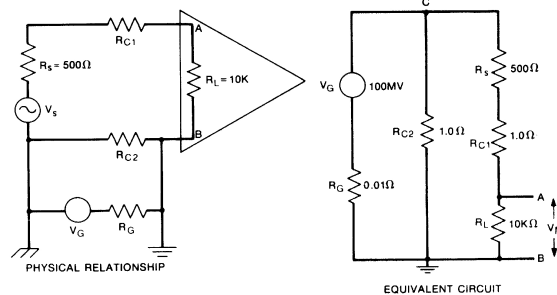


Figure 3-16. With two ground connections, much of the ground-potential difference appears across the load as noise.

Alternative 2: One ground connection

Signal source is not grounded (almost): Z_{SG} is a parasitic large impedance.

When

$$R_{C2} \ll R_S + R_{C1} + R_L$$

and

$$Z_{SG} \gg R_{C2} + R_G$$

we have that

$$V_N = \left[\frac{R_L}{R_L + R_{C1} + R_S} \right] \left[\frac{R_{C2}}{Z_{SG}} \right] V_G$$

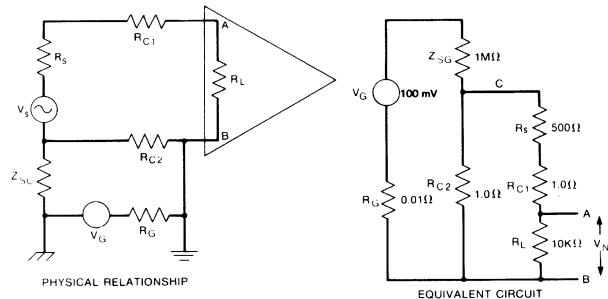


Figure 3-17. A large impedance between the source and ground keeps most of the ground-potential difference away from the load and reduces noise.

Example:

Same values as in the previous example plus:

$$Z_{SG} = 1 \text{ M}\Omega$$

$$\Rightarrow V_N = 0.095 \mu\text{V}$$

Shielded, packaged amplifiers

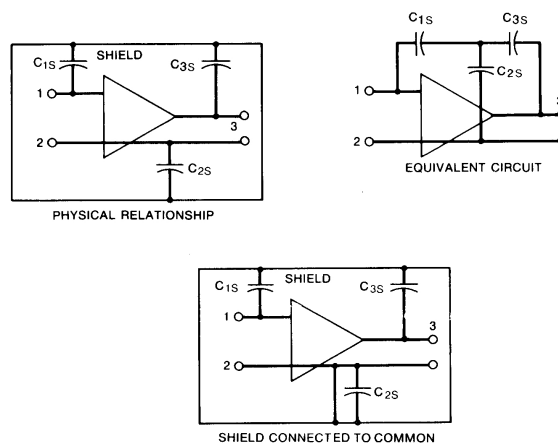


Figure 3-18. Amplifier shield should be connected to the amplifier common.

If the house is not properly grounded it may be a part of a unwanted feedback and result in instability. Proper grounding is illustrated at the bottom figure. Here the package house is coupled to the common input/output reference ground.

How to ground the shield?

Case 1: When only the AMP is grounded.

A: Shield noise will return through one of the signal wires. This is the worst case.

Prioritised order: C, D, B, and A.

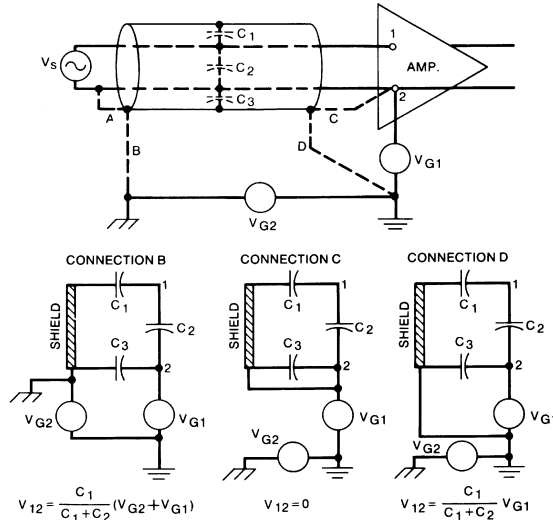


Figure 3-19. When amplifier is grounded, the best shield connection is C, with shield connected to amplifier common.

How to ground the shield?

Case 2: When only the signal source is grounded.

C: Shield noise will return through one of the signal wires. This is the worst case in this setup.

Prioritised order: A, B, D and C.

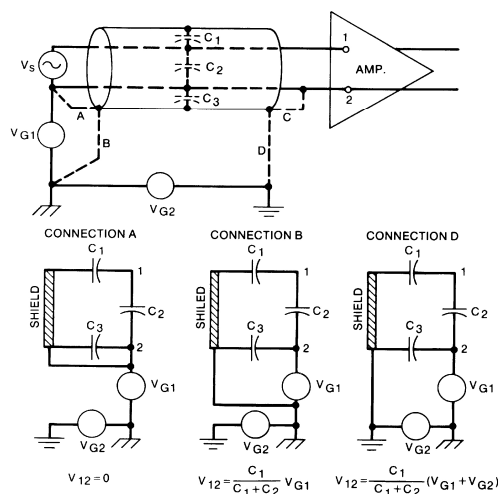


Figure 3-20. When source is grounded, the best shield connection is A, with shield connected to the source common. The configuration can also be used with a differential amplifier.

3.4 GROUND LOOPS

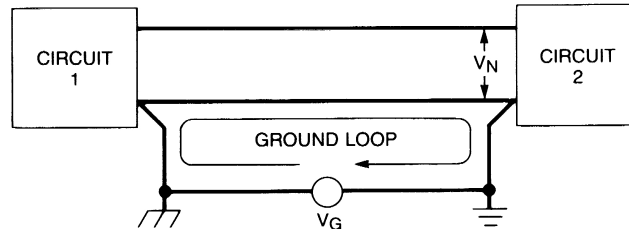


Figure 3-22. A ground loop between two circuits.

By “ground loop” we mean a closed loop where the potential ideally should have been at ground all over the loop. However there may be running a current in this loop influencing significantly on the electronic circuitry. There are two main causes for currents in ground loops: The current may be due to magnetic fields or due to large passing currents in part of the ground loop say in a ground plan.

Countermeasures depending on cause:

1. Reduce the size of the loop (if magnetic cause)
2. Route the current in a different direction (if passing current).

Cause independent countermeasures:

1. Change the system to only one ground connection.
2. "Split" the loop electronically
 - a) transformer
 - b) common mode choke
 - c) optical coupler
 - d) balanced circuit
 - e) frequency selective grounding (hybrid ground).

a) Transformer

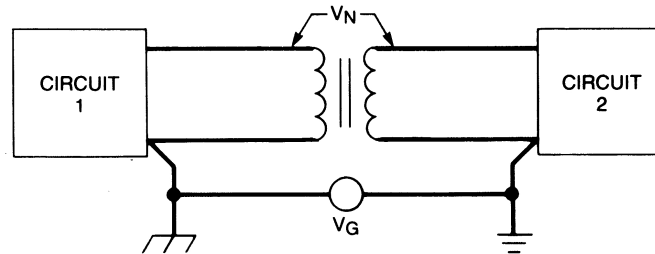


Figure 3-23. A ground loop between two circuits can be broken by inserting a transformer.

The noise is over the trafo and will not influence on the differential voltage. Capacitive coupling may give some noise infection. This coupling may be reduced by shielding the trafo.

b) Common mode choke

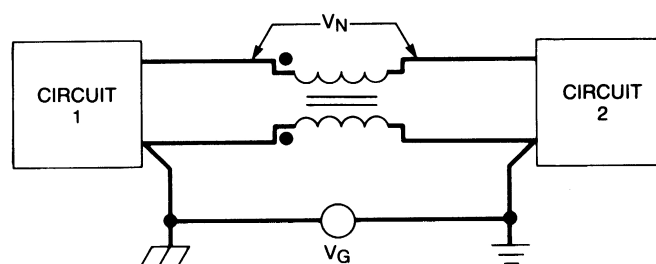


Figure 3-24. A ground loop between two circuits can be broken by inserting a common-mode choke.

(To be discussed in detail a little later.)

c) Optical coupler

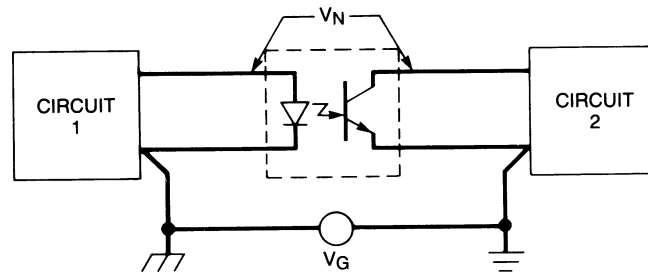


Figure 3-25. An optical coupler can be used to break the ground loop between two circuits.

An attractive alternative when the ground voltage difference is very large. It is better suited for digital circuitry than analogue circuitry due to bad linearity.

d) Balanced circuit

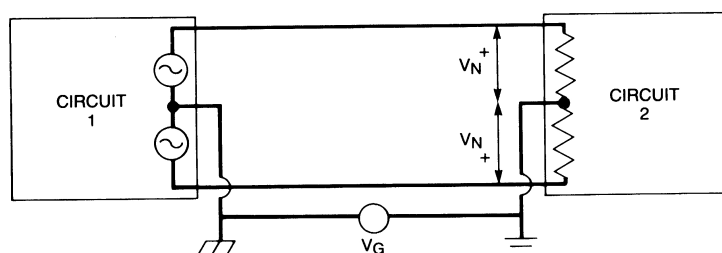


Figure 3-26. A balanced circuit can be used to cancel out the effect of a ground loop between two circuits.

If the ground current was equally divided into the two differential lines, the noise will be eliminated in the receiver. Hence the efficiency will depend on how well symmetry we manage to achieve.

3.5 LOW-FREQUENCY ANALYSIS OF COMMON-MODE CHOKE

Other names used:
longitudinal choke,
neutralizing transformer,
balun.

Signal current: Current in
opposite directions in the
differential pair. Low
impedance.

Common mode current:
Current in the same direction
in both differential conductors.
High impedance.

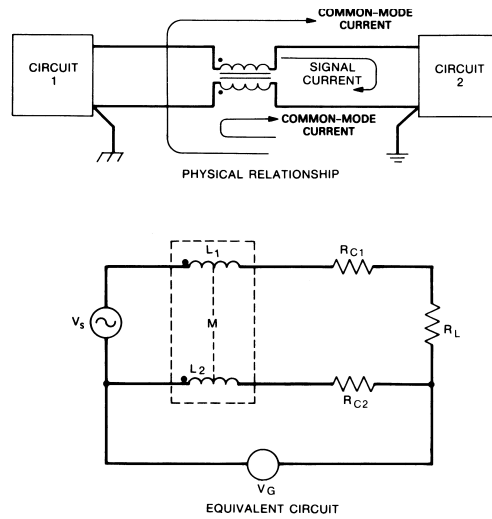


Figure 3-27. When dc or low-frequency continuity is required, a common-mode choke can be used to break a ground loop.

Calculation of signal current

(Ref: similarities with previous equation (2-22))

When f is over R_{C2}/L_2 most of the return current will pass through the other differential conductor. When f is over $5R_{C2}/L_2$ we have that approximately all current passes through the other line and nothing through ground.

Now we can put up the following equation:

$$V_s = j\omega(L_1 + L_2)I_s - 2j\omega MI_s + (R_L + R_{C2})I_s$$

If the coils are approximately equal and are on the same kernel, we have that: $L_1 = L_2 = M$

Then we have: $I_s = \frac{V_s}{R_L + R_{C2}} \approx \frac{V_s}{R_L}$ given that $R_L \gg R_{C2}$

NB! Without choke we get the same expression.

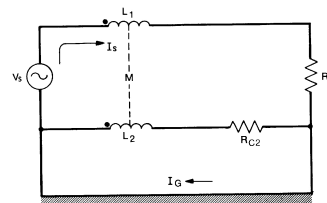


Figure 3-28. Equivalent circuit for Fig. 3-27 for analysis of response to signal voltage V_s .

I.e. the choke does not have any influence on the signal current when the frequency is over $5R_{C2}/L_2$. Hence we will try to choose R_{C2} and L_2 so that the corner frequency becomes lower than the lowest possible signal frequency.

Estimates of common noise current

The current in the outer loop is: $V_G = j\omega L_1 I_1 + j\omega M I_2 + I_1 R_L$
 while the current in the inner loop is: $V_G = j\omega L_2 I_2 + j\omega M I_1 + R_{C2} I_2$

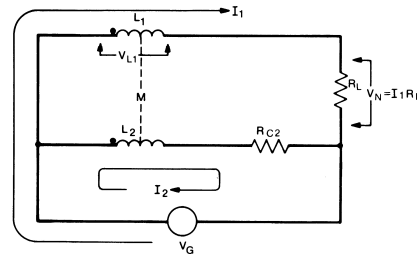


Figure 3-29. Equivalent circuit for Fig. 3-27 for analysis of response to common-mode voltage V_G .

We find I_2 from the last expression:

$$I_2 = \frac{V_G - j\omega M I_1}{j\omega L_2 + R_{C2}}$$

We still assume $L_1 = L_2 = M$ and include the last expression in the expression for the current in the outer loop and achieve:

$$I_1 = \frac{V_G R_{C2}}{j\omega L(R_{C2} + R_L) + R_{C2} R_L}$$

$$I_1 = \frac{V_G R_{C2}}{j\omega L(R_{C2} + R_L) + R_{C2} R_L}$$

The noise voltage V_N is equal to $I_1 R_L$. Since R_{C2} typically is much less than R_L we may remove the first term in the parenthesis and ends up with:

$$V_N = \frac{V_G R_{C2} / L}{j\omega + R_{C2} / L}$$

To minimize the part of the noise voltage that reaches the "receiver" R_{C2} should be as small as possible and the choke inductance should be so that $L \gg \frac{R_{C2}}{\omega}$ where ω is the frequency of the noise.

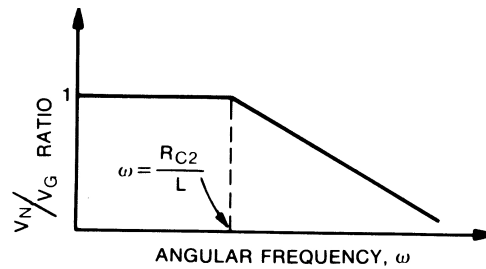


Figure 3-30. Noise voltage may be significant if R_{C2} is large.

The figure below shows an example of how this can be done.

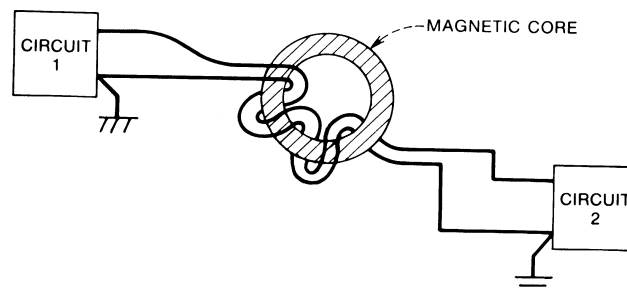


Figure 3-31. An easy way to place a common-mode choke in the circuit is to wind both conductors around a toroidal magnetic core. A coaxial cable may also be used in place of the conductors shown.

Differential amplifiers

- Differential amplifiers (top figure) have less sensitivity to common mode noise. However it is also possible to achieve this with a single sided amplifier if connected as shown in the bottom figure below.
- Both the real differential and the one based on the single sided amplifier can be represented by the same equivalent schematic and the same equation.

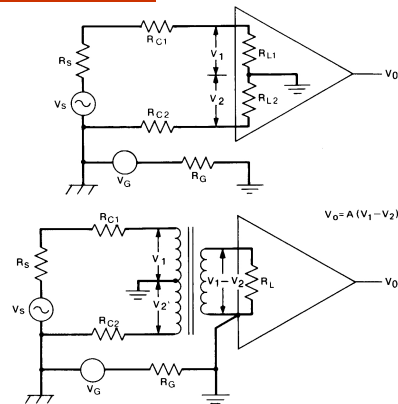


Figure 3-35. A differential amplifier—or a single-ended amplifier with transformer—can be used to reduce the effects of a common-mode noise voltage.

If we assume that R_{L2} is much larger than R_G we can simplify to the following equation:

$$V_N = V_1 - V_2 = \left(\frac{R_{L1}}{R_{L1} + R_{C1} + R_S} - \frac{R_{L2}}{R_{L2} + R_{C2}} \right) V_G$$

Example:

$$V_G = 100\text{mV}$$

$$R_G = 0.01\Omega$$

$$R_S = 500\Omega$$

$$R_{C1} = R_{C2} = 1\Omega$$

$$\text{If } R_{L1} = R_{L2} = 10\text{k}\Omega \text{ then } V_N = 4.6\text{mV}$$

$$\text{If } R_{L1} = R_{L2} = 100\text{k}\Omega \text{ then } V_N = 0.5\text{mV}$$

Larger R_L and/or smaller R_S is attractive

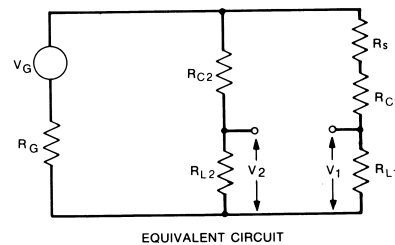


Figure 3-36. Equivalent circuit for analysis of differential-amplifier circuit.

- It is possible to increase the input impedance for the common mode signal without increasing the impedance experienced by the differential signal. This can be achieved by inserting a resistance R as drawn in the figure.

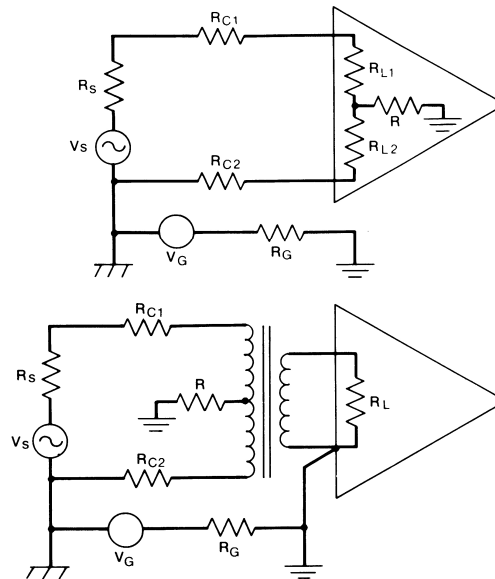


Figure 3-37. Insertion of resistance R into ground lead decreases the noise voltage.

Guard shields

In general we have that $(R_s + R_1 + X_{C1G}) <> (R_2 + X_{C2G})$. The difference in the ground potential V_G will result in two different currents through the differential pair and thus two different voltage drops over X_{C1G} and X_{C2G} even though X_{C1G} and X_{C2G} are equal.

To make the currents equal $(R_s + R_1 + X_{C1G}) = (R_2 + X_{C2G})$ at the same time as $X_{C1G} = X_{C2G}$. A simpler solution is to try to make the voltage drop over the differential wires equal to 0V. If so the voltage drop over the inputs become equal (i.e. 0V).

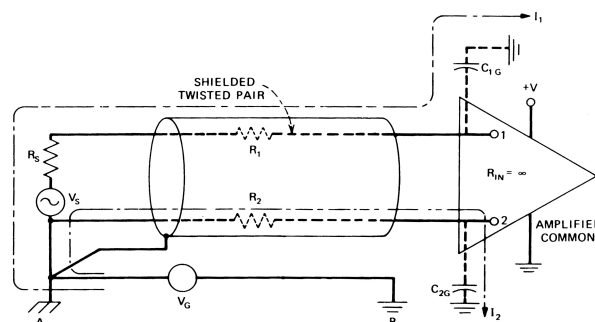


Figure 3-39. Amplifier and a grounded source are connected by a shielded twisted pair.

$$V_{in}(x) = \frac{Z_{in}(x)}{Z_{in}(x) + Z_{rest}(x)} V_{fellesstoy}$$

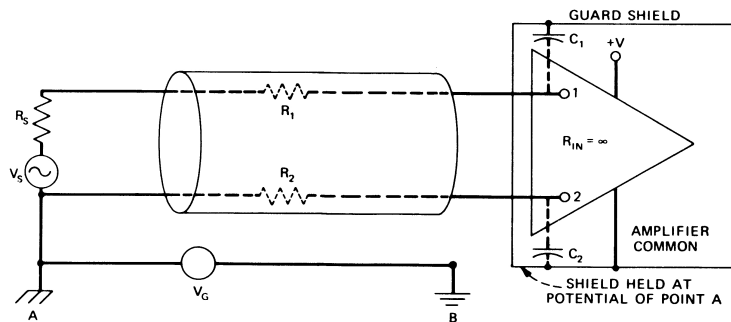


Figure 3-40. Guard shield at potential of point A eliminates noise currents.

In the solution drawn above we have a screen encapsulating the amplifier. The shield is connected so that it has the same ground potential as the source (point A). In this way the ground voltage drop will be zero from point A, through the differential wires and through the amplifier input towards the shield.

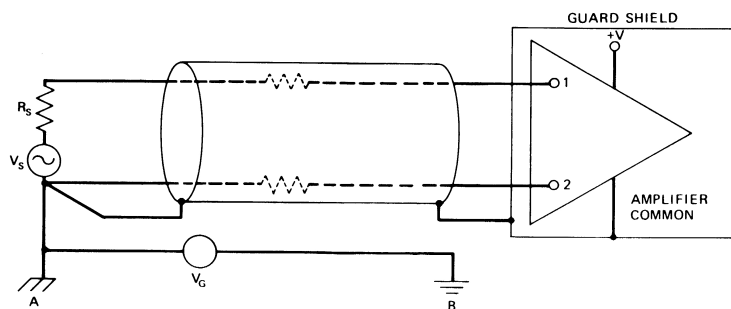


Figure 3-41. Guard shield is connected to point A through the cable shield.

The figure illustrates how the amplifier shield can be connected to point A via the cable shield.

The amplifier power source can not refer to point B. Possible power options are via cable from A, having an independent power source (say a battery) or coupled via a galvanic element to the power source on the right side.

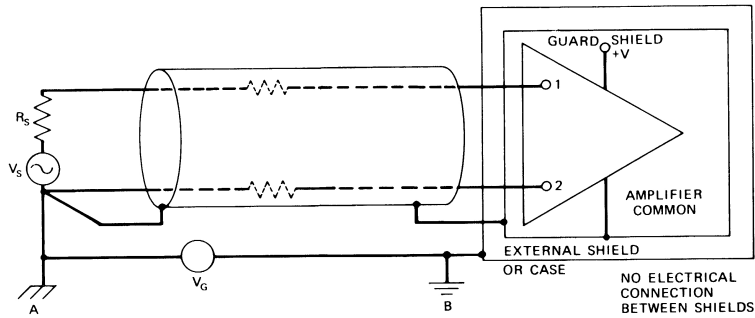


Figure 3-42. Practical circuit often has a second shield around the guard shield.

If it is likely/a possibility that the screen encapsulating the amplifier can pick up noise from the surroundings a double shield may be a possibility. In this case the outer shield is grounded locally and it is also important that the impedance between the two shields are high enough compared with the other influencing impedances in the system.

Example:

$V_G = 100\text{mV}$ at 60Hz, $R_1 = R_2 = 0$, $R_S = 2.6\text{k}\Omega$,

$C_{1G} = C_{2G} = 100\text{pF} \Rightarrow X_C = 26\text{M}\Omega$ at 60Hz

a) Without amplifier shield

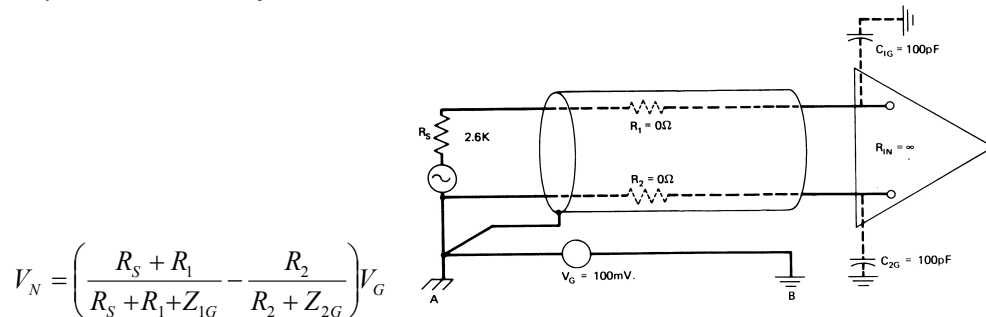


Figure 3-43. Numerical example to illustrate need for guard shield.

Given the values above we achieve: $V_N = 10\mu\text{V}$

b) With amplifier shield:

Assume that the shield results in a change of C_{1G} and C_{2G} from 100pF to 2pF. We may use the same expression as above and now have: $V_N = 0.2\mu V$
i.e. now an attenuation of 34 dB

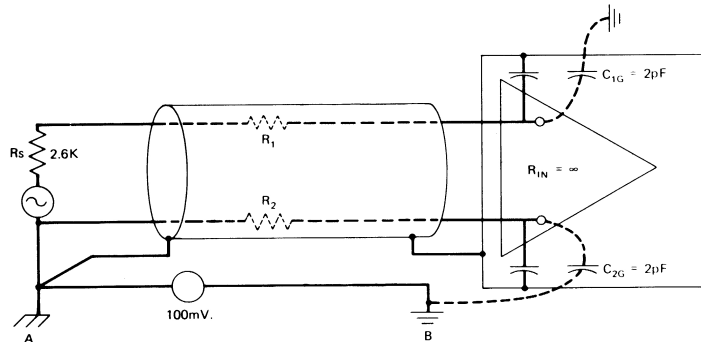


Figure 3-44. Guard shield reduces line capacitance to ground and therefore noise voltage.

Measuring apparatus with "Guard". Discussion of alternative connections

- How to connect "Guard" to achieve the best possible measuring results?

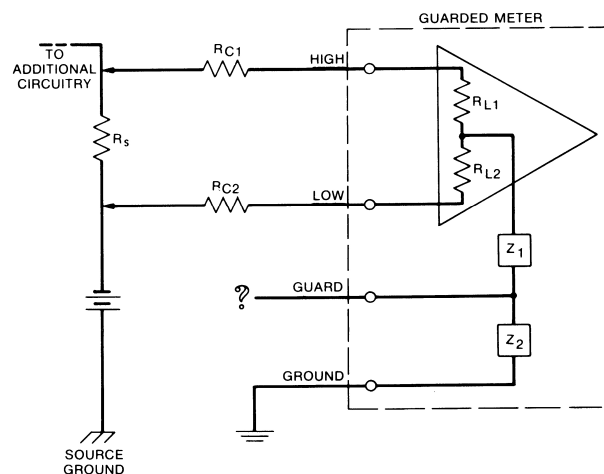


Figure 3-45. When a guarded meter is used, a common problem is where to connect the guard terminal.

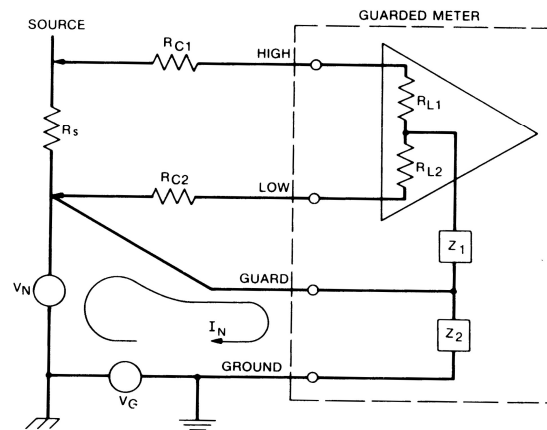


Figure 3-46. When measuring voltage across R_s , best connection for the guard is to the low-impedance side of R_s ; noise current does not affect amplifier.

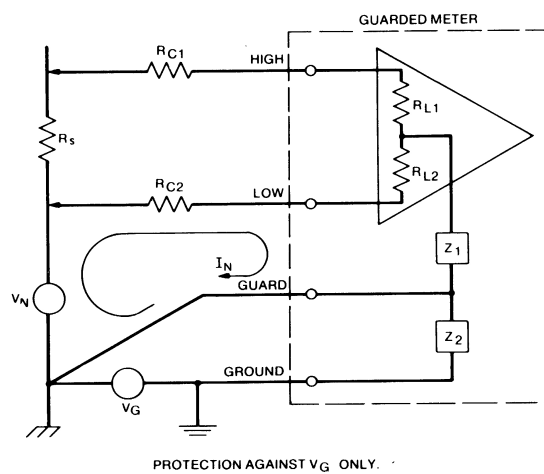


Figure 3-47. Guard connected to source ground gives no protection against V_N .

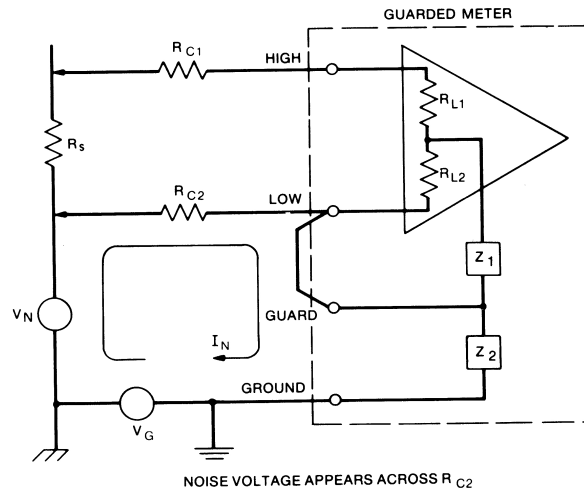


Figure 3-48. Guard connected to low side of meter allows noise current to flow in line resistance R_{C2} .

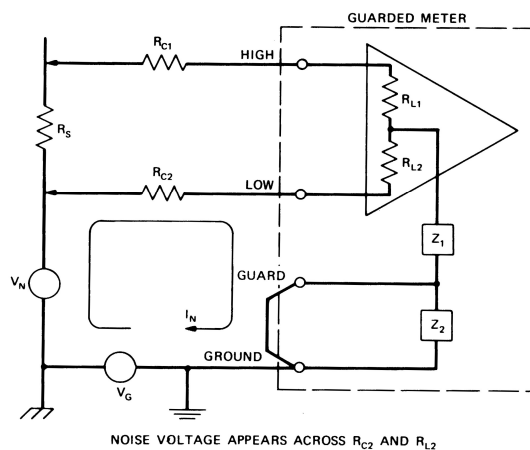


Figure 3-49. Guard connected to local ground is ineffective; noise current flows through R_{C2} , R_{L2} , and Z_1 .

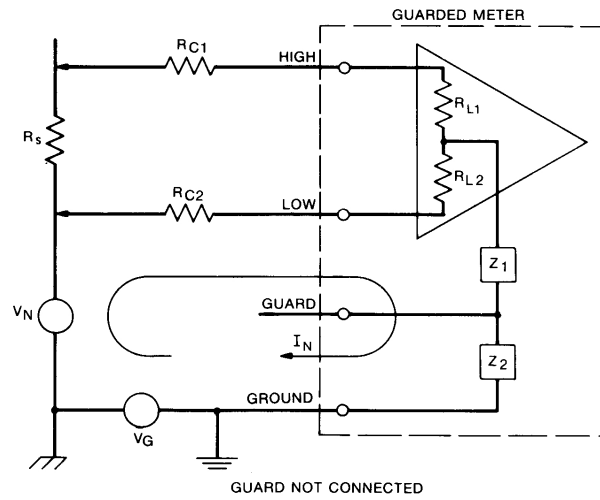


Figure 3-50. Guard not connected; noise currents due to V_N and V_G flow through R_{C2} , R_{L2} , Z_1 , and Z_2 .