

LAB 2 - INF3410

AKSEL KVALHEIM JOHNSBY, ERLEND OFSTAD NORENDAL, KARL ERIK KIBUR

1. TASK 1



```

1 %Oppgave 1.1 Vgs-sweep%
2
3 betaP=55*(10^-6);%P-type
4 betaN=190*(10^-6);%N-type
5 Vtn=0.57;
6 Vtp=0.71;
7 lambda=0.16;
8 VTemp=26*(10^(-3));
9 n=1;
10
11 Vgs=linspace(0,3.3,50);
12 Is= 2*n*betaN*(VTemp^2);
13 Vs=0;
14 Vd=1;
15 %Idmax=2.832mA
16 %For active region Vds>Vgs-Vtn
17 %For triode region 0<Vds<Vgs-Vtn
18
19 for i=1: length(Vgs)
20 If(i)=Is*(log(1+exp((Vgs(i)-Vtn-n*Vs)/(n*VTemp)))^2)*(1+
    lambda*Vs);
21 Ir(i)=Is*(log(1+exp((Vgs(i)-Vtn-n*Vd)/(n*VTemp)))^2)*(1+
    lambda*Vd);
22 Id(i)=If(i)-Ir(i);
23 end
24
25 figure(1);
26 plot(Vgs,Id);
27 xlabel('Vgs(V)');
28 ylabel('Id(A)');
29 grid on;
30 figure(2);
31 semilogy(Vgs, Id);
32 xlabel('Vgs(V)');
33 ylabel('log(Id) (A)');
34 grid on;

```



Matlab code used for task 1.1 and 1.2

Task 1.1

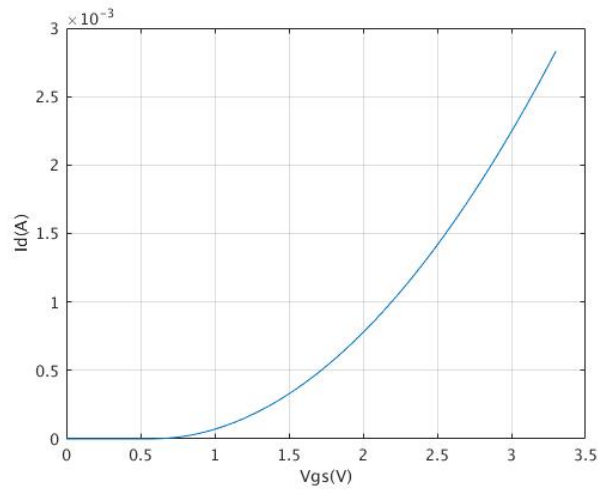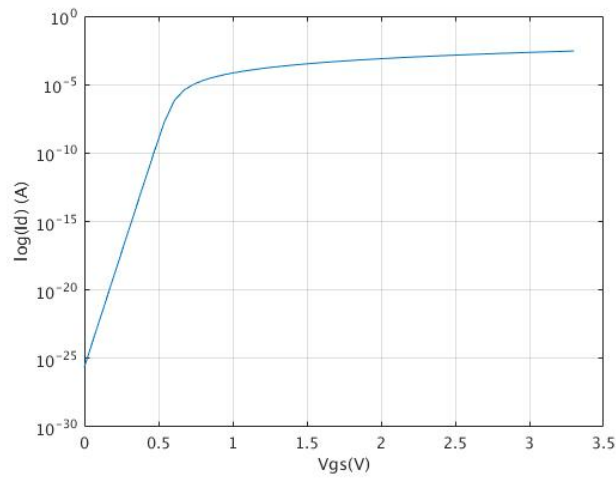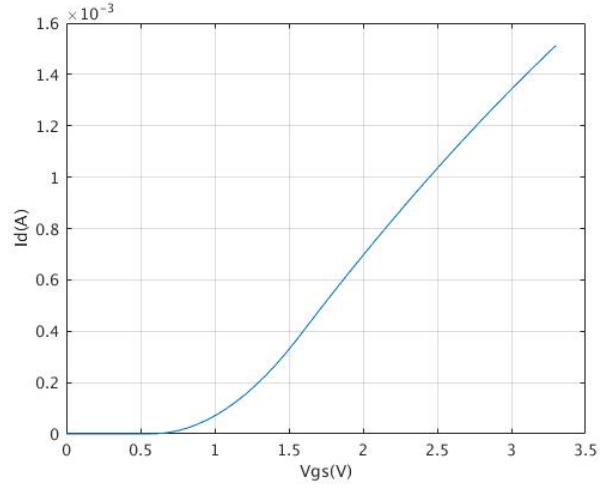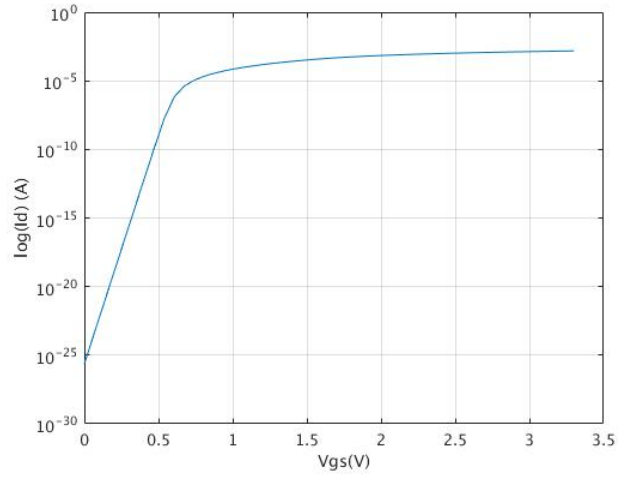FIGUR 1. Linear plot of V_{gs} as a function of I_d FIGUR 2. Log plot of V_{gs} as a function of I_d

As long as $V_{ds} > V_{ov}$ the transistor will be in the active region. As long as $V_{gs} < V_{tn}$ the transistor is off. This means that the active region is when $V_{gs} > V_{tn}$. V_d is set higher than $V_{gs(max)}$. That means that no matter how high we set V_{ds} , I_{ds} does not get higher than approx. 2.8mA.

Task 1.2

FIGUR 3. Linear plot of V_{gs} as a function of I_d FIGUR 4. Log plot of V_{gs} as a function of I_d

To ensure that the curve is in the triode region $V_{ov} > V_{ds}$. The transistor needs to be turned on ($V_{gs} > V_{tn}$) for it to be in the triode region.


```

1 %Oppgave 1.1 Vgs-sweep%
2 clear all;
3 betaP=55*(10^-6);%P-type
4 betaN=190*(10^-6);%N-type
5 Vtn=0.57;
6 Vtp=0.71;
7 lambda=0.16;
8 VTemp=26*(10^(-3));
9 n=1;
10
11 Vgs=linspace(Vtn-0.1,Vtn+0.1,6);
12 Is= 2*n*betaN*(VTemp^2);
13 Vd=linspace(0,3.3,100);
14 Vs=0;
15 %Idmax=2.832mA
16 %For active region Vds>Vgs-Vtn
17 %For triode region 0<Vds<Vgs-Vtn
18 for j=1: length(Vgs)
19     Vov(j)=Vgs(j)-Vtn;
20     for i=1: length(Vd)
21         If(i)=Is*(log(1+exp((Vgs(j)-Vtn-n*Vs)/(n*VTemp)))
22             ^2)*(1+lambda*Vs);
23         Ir(i)=Is*(log(1+exp((Vgs(j)-Vtn-n*Vd(i))/(n*VTemp
24             )))^2)*(1+lambda*Vd(i));
25         Id(i)=If(i)-Ir(i);
26         if Vd(i)-Vov(j)<0.05
27             Sat(j)=Id(i);
28         end
29     end
30     plot(Vd,Id);
31     xlabel('Vds(V)');
32     ylabel('Id(A)');
33     grid on;
34     hold on;
35 end
36 %plot(Vov,Sat);
37 legend('0.46V','0.51V','0.55V','0.59V','0.63V','0.67V','
38     Location','northeast');

```

Matlab code used for task 1.3 and 1.4

Task 1.3

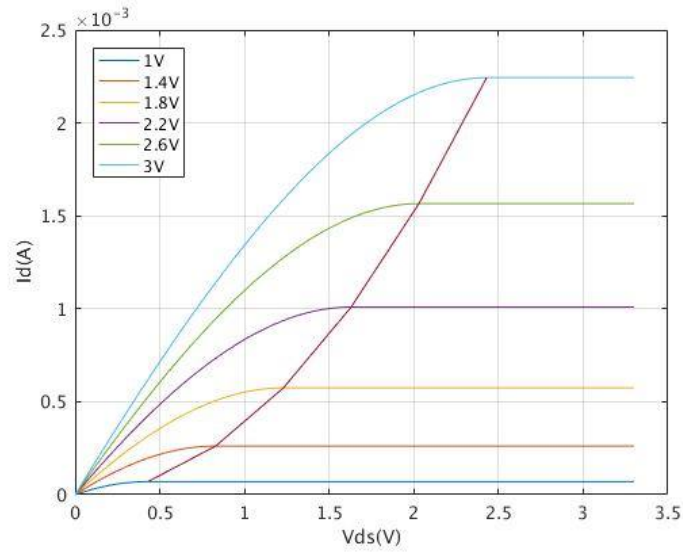

FIGUR 5. Plot of different voltages for V_{gs} . The line that grows exponentially marks where:

$$V_{ds} - V_{ov} < 50mV$$



This means that every point left of the line is in triode region and every point right of the line is in saturation.

Task 1.4

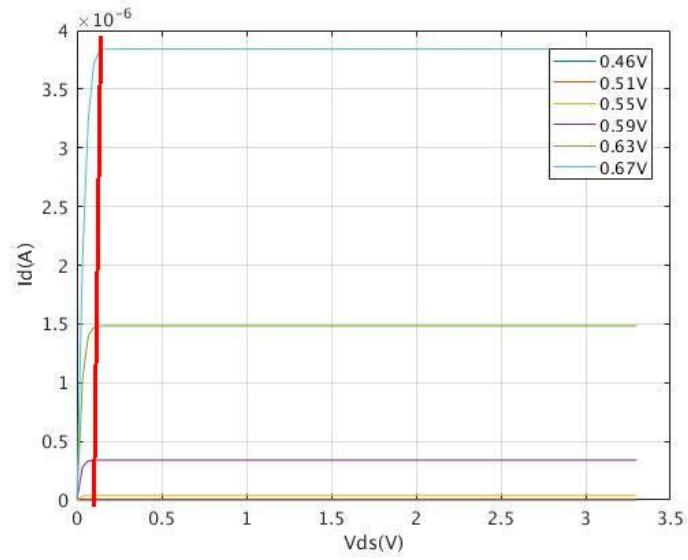
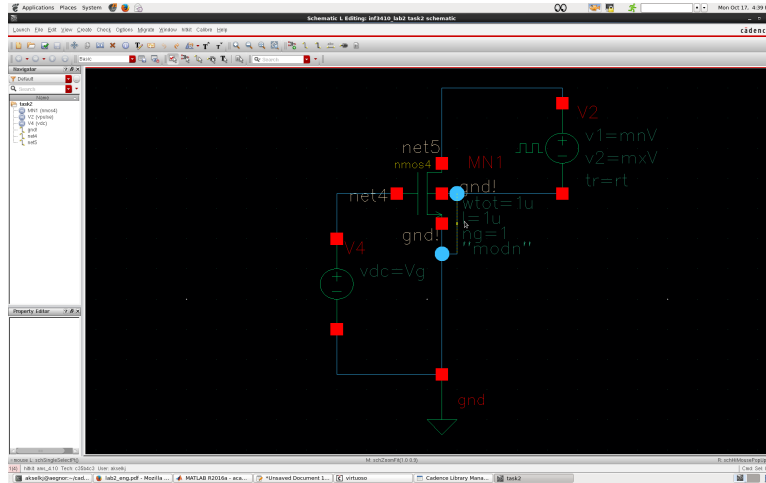
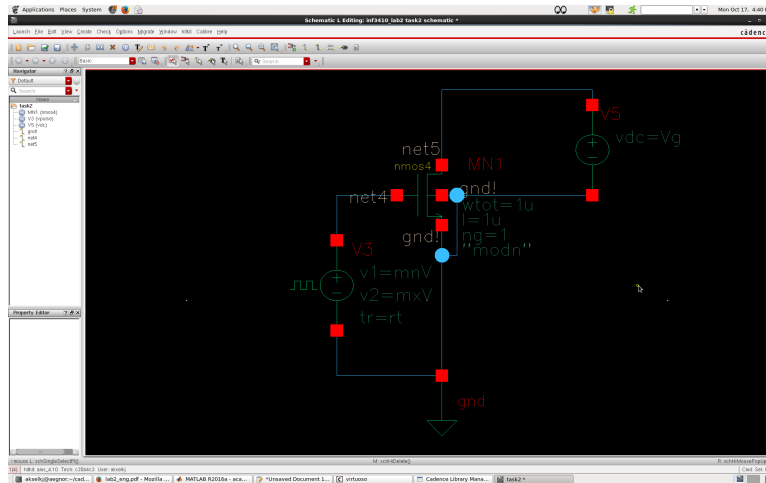


FIGURE 6. To ensure that the curve is in weak inversion we sweep V_{gs} within ± 100 mV of V_{tn} . The constant behaviors is due to the EKV-model being inaccurate at this voltage range.

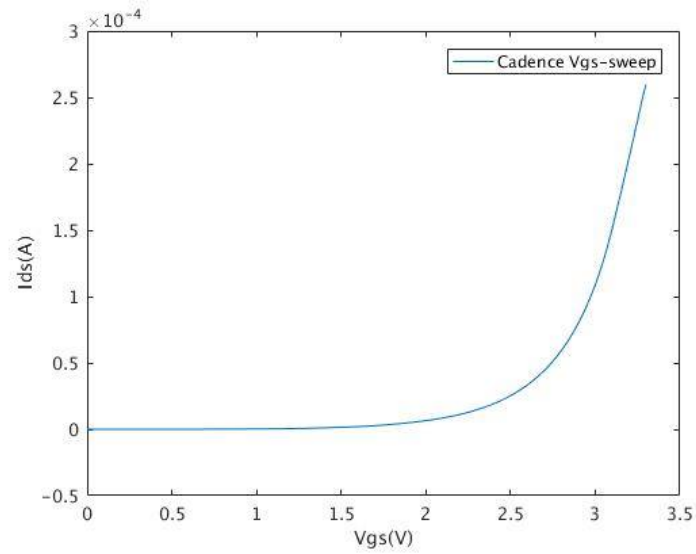
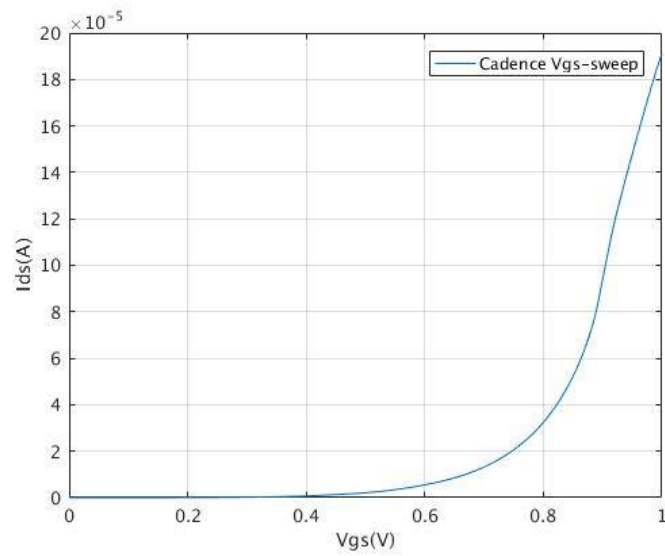
2. Task 2


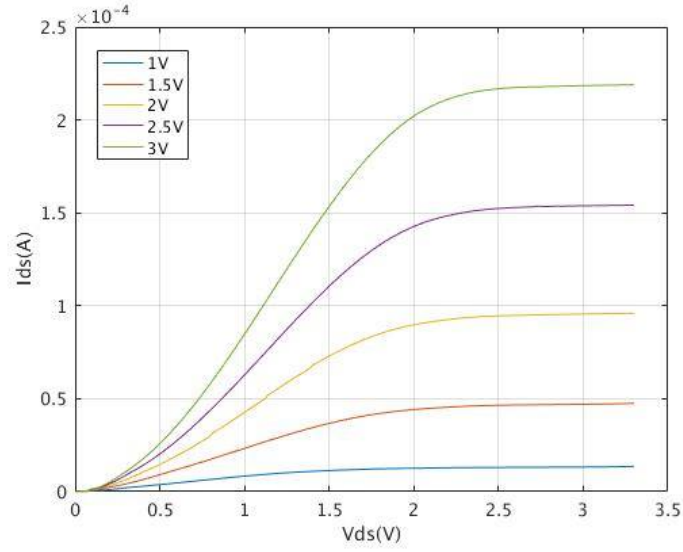


FIGUR 7. V_{ds} sweep configuration in cadence.

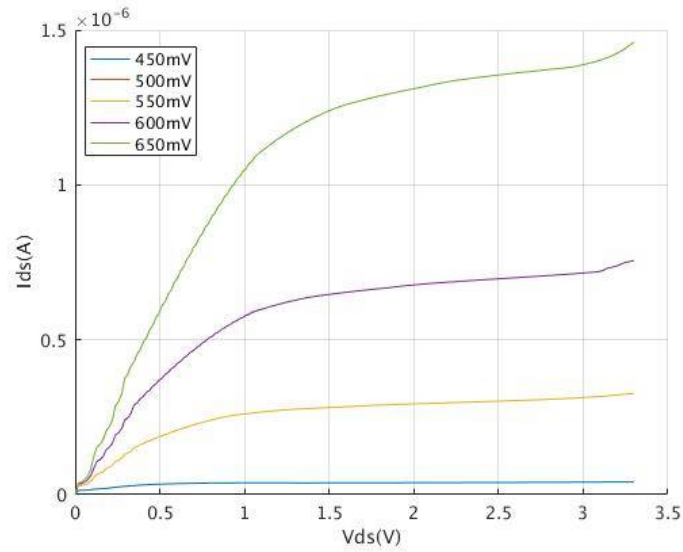

FIGUR 8. V_{gs} sweep configuration in cadence.

FIGURE 9. Cadence V_{gs} sweep of the saturation region (Linear).FIGURE 10. Cadence V_{gs} sweep of the triode region (Linear).

FIGUR 11. Cadence V_{ds} sweep of the strong inversion (Linear).FIGUR 12. Cadence V_{ds} sweep of the weak inversion (Linear).


In the weak inversion plot we had some problems with plotting 450mV and 550mV. Somehow we got the same plot for the two, although the numbers provided by cadence was different from each other.




3. TASK 3

```
1 %Oppgave 3
2 betaP=55*(10^-6);%P-type
3 betaN=185*(10^-7);%N-type
4 Vtn=0.57;
5 Vtp=0.72;
6 lambda=0.71;
7 VTemp=26*(10^(-3));
8 n=1;
9 Vgs=3;
10 Is= 2*n*betaN*(VTemp^2);
11 Vd=linspace(0,3.3,100);
12 Vs=0;
13 %For active region Vds>Vgs-Vtn
14 %For triode region 0<Vds<Vgs-Vtn
15 for j=1: length(Vgs)
16     Vov(j)=Vgs(j)-Vtn;
17     for i=1: length(Vd)
18         If(i)=Is*(log(1+exp((Vgs(j)-Vtn-n*Vs)/(n*VTemp)))
19             ^2)*(1+lambda*Vs);
20         Ir(i)=Is*(log(1+exp((Vgs(j)-Vtn-n*Vd(i))/(n*VTemp
21             )))^2)*(1+lambda*Vd(i));
22         Id(i)=If(i)-Ir(i);
23         if abs(Vd(i)-Vov(j))<0.5
24             Sat(j)=Id(i);
25         end
26     end
27     plot(Vd,Id);
28     xlabel('Vds(V)');
29     ylabel('Id(A)');
30     grid on;
31     hold on;
32 end
33 hold on;
34 %plot(Oppgave2c_xaksel,Oppgave2c1vgs);
35 %plot(Oppgave2c_xaksel,Oppgave2c15vgs);
36 %plot(Oppgave2c_xaksel,Oppgave2c2vgs);
37 %plot(Oppgave2c_xaksel,Oppgave2c25vgs);
38 plot(Oppgave2c_xaksel,Oppgave2c3vgs);
39 grid on;
40 legend('EKV-model','Cadence','location','northwest');
41 hold off;
```

Our matlab code used in Task 3. Ofcourse with some changes throughout the task.

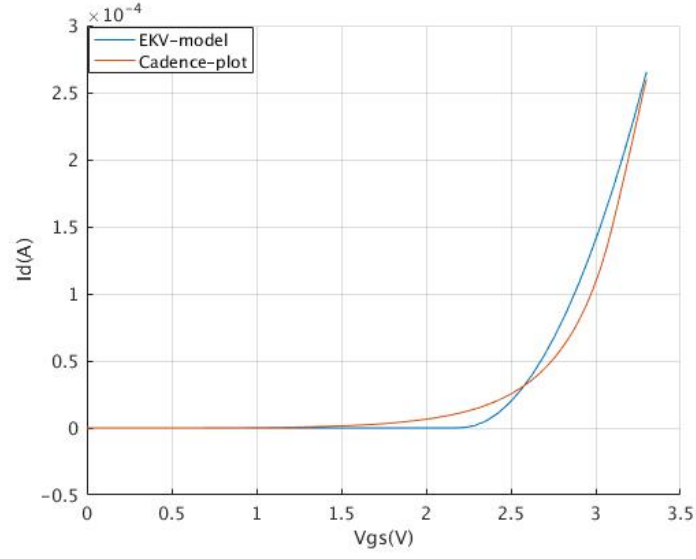

FIGUR 13. Changed values in EKV-model: $\beta_N = 900 \cdot 10^{-7}$, $V_{tn} = 2.2V$, $\lambda = 0.14$, $n = 1.2$.

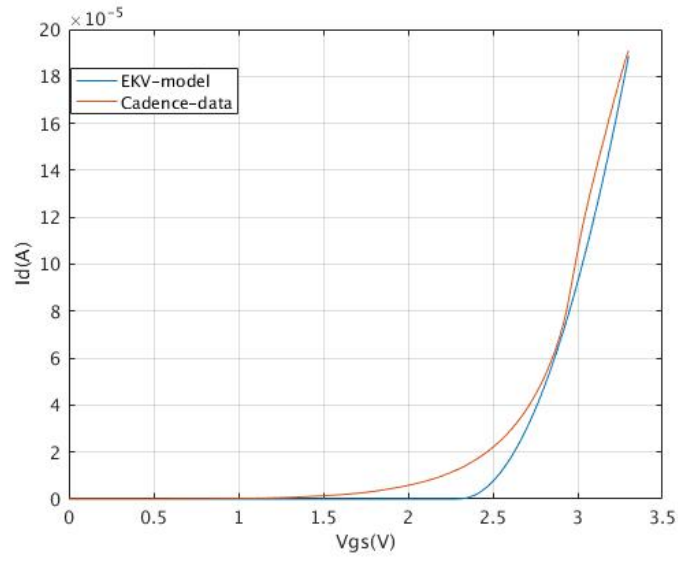

FIGUR 14. Changed values in EKV-model: $\beta_N = 80 \cdot 10^{-6}$, $V_{tn} = 2.3V$, $\lambda = 0.18$, $n = 1$.

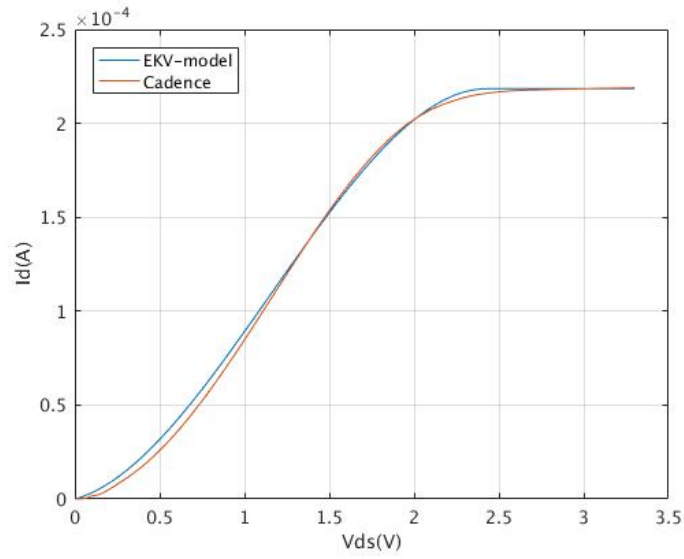


FIGURE 15. Changed values in EKV-model: $\beta_N = 185 \times 10^{-7}$, $V_{tn} = 0.57V$, $\lambda = 0.71$, $n = 1$, $V_{gs} = 3V$

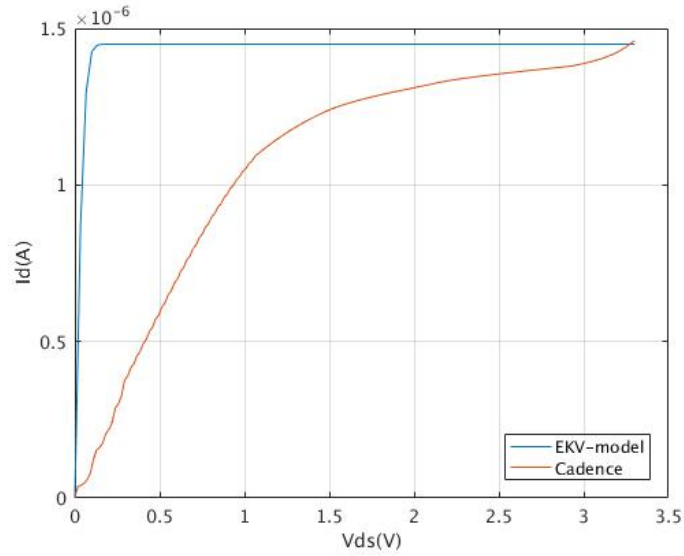


FIGURE 16. Because of the knee points, it was difficult to make the EKV-model fit the cadence simulations. Changes done in EKV-model: $\beta_N = 110 \times 10^{-6}$, $\lambda = 1$, $V_{gs} = 0.65V$




4. TASK 4

```


1 clear all;
2 addpath(genpath('/hom/mes/src/matlab/gpib/linux'));
3 HPE3631_Init;
4 K617_Init;
5 K617_SetMode('A');
6
7 Vdd=3.3;
8 Vgs=linspace(0,3.3,40);
9 HPE3631_SetVolt(1,Vdd);
10 %Idmax=1.442 Vdd=0.5
11 %Idmax=2.387 Vdd=1
12 %Idmax=3.002 Vdd=2
13 %Idmax=3.125 Vdd=4
14 %Idmax=3.206 Vdd=8
15 %Idmax=3.264 Vdd=12
16
17
18
19
20 for i=1: length(Vgs)
21     HPE3631_SetVolt(2,Vgs(i));
22     pause(0.05);
23     Ids(i)= K617_ReadQuick;
24 end
25 HPE3631_SetVolt (1, 0);
26 HPE3631_SetVolt (2, 0);
27 HPE3631_SetVolt (3, 0);
28
29
30
31
32
33 figure(1);
34 plot(Vgs,Ids);
35 xlabel('Vgs(V)');
36 ylabel('Id(A)');
37 grid on;
38 %{
39 figure(2);
40 semilogy(Vgs, Ids);
41 xlabel('Vgs(V)');
42 ylabel('log(Id) (A)');
43 grid on;
44 %}

```


Matlab code used for the first two plots in task 4.

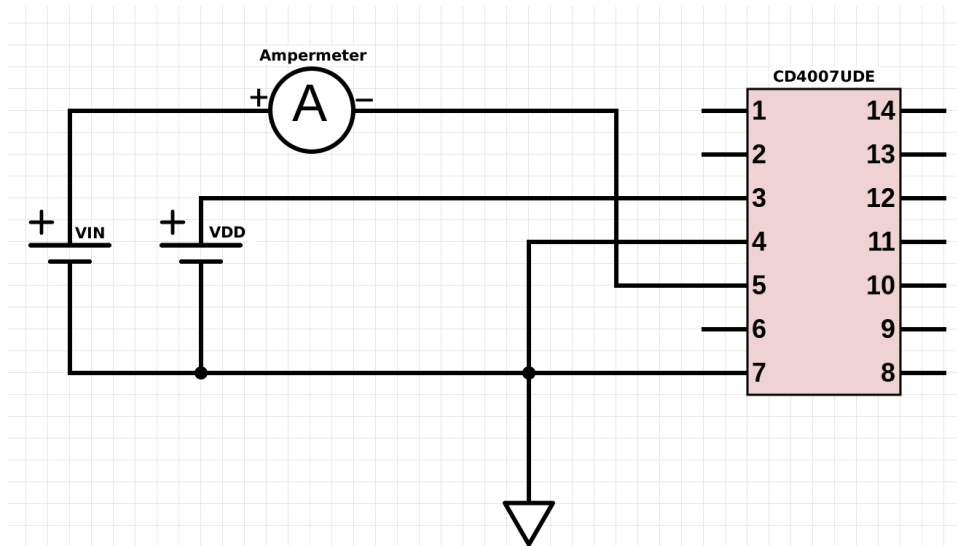


FIGUR 17. How we connected our circuit in Task 4. Voltage range is from 0V to 3.3V. Power is 3.3V.

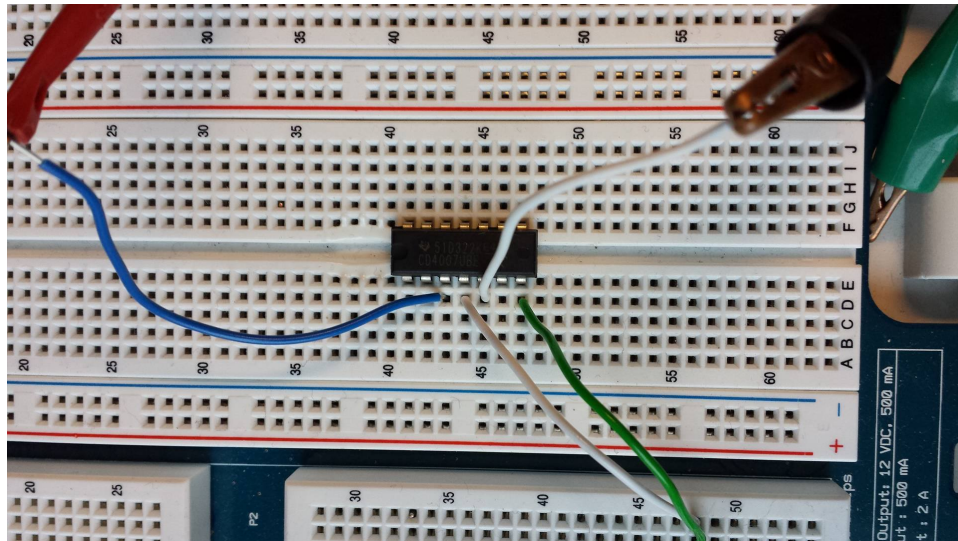


FIGUR 18. Elvis board setup.

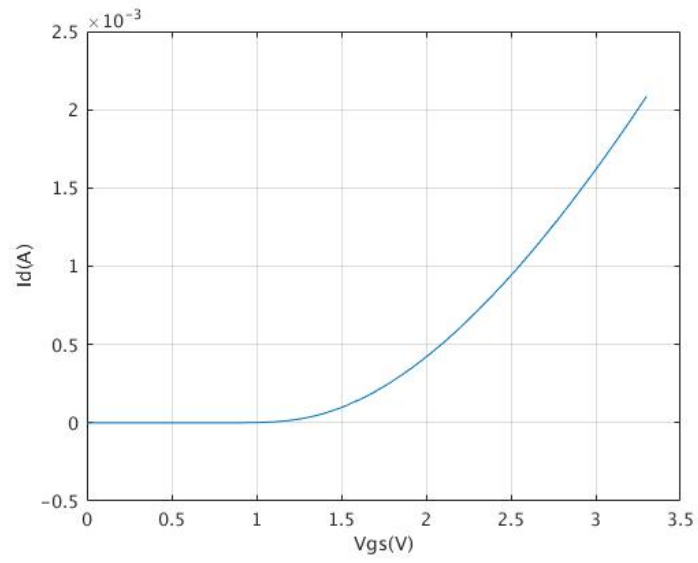


FIGUR 19. Sweep in the active region (Linear)

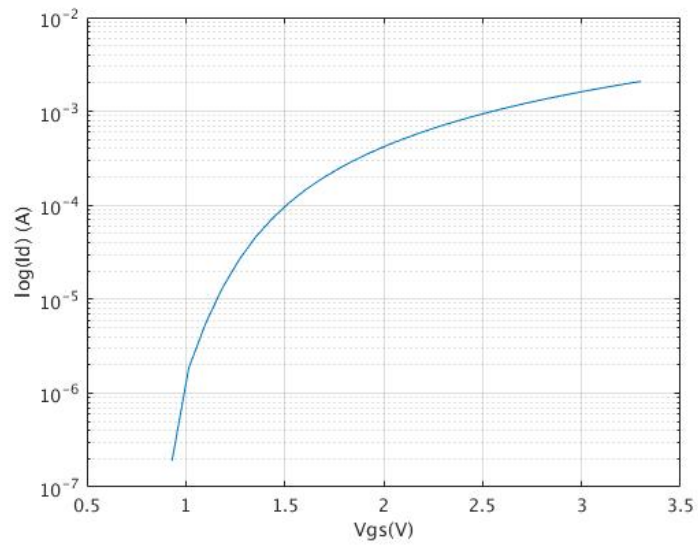


FIGUR 20. Sweep in the active region (Logarithmic)

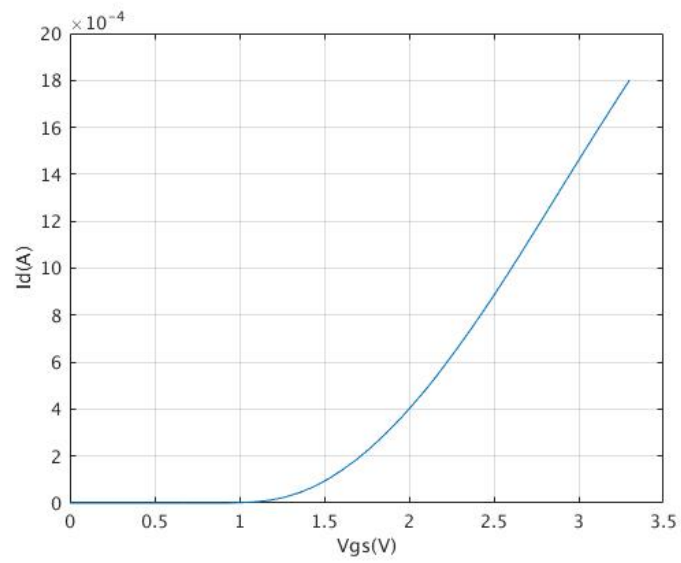

FIGUR 21. Sweep in triode region (Linear)

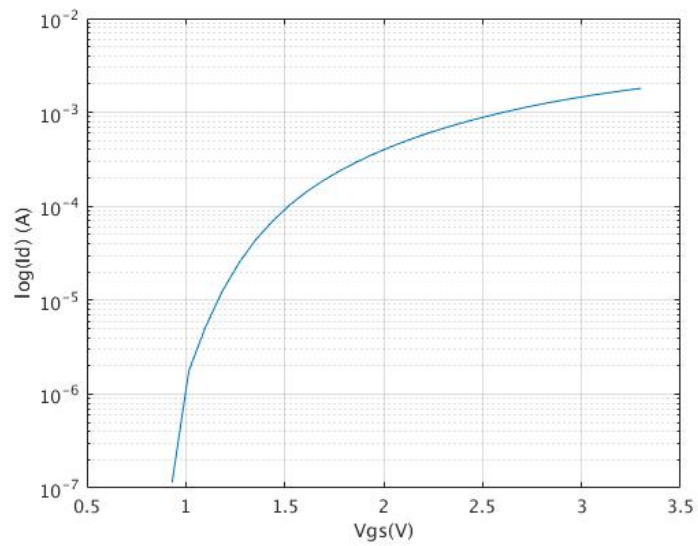

FIGUR 22. Sweep in triode region (Logarithmic)

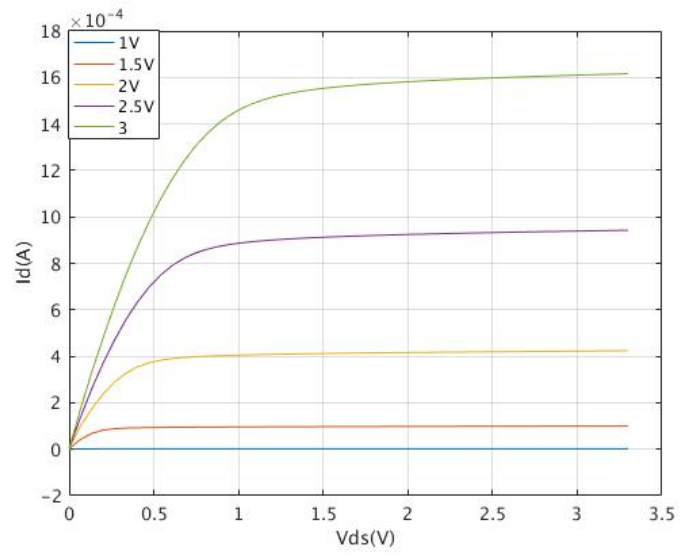

FIGUR 23





5. TASK 5

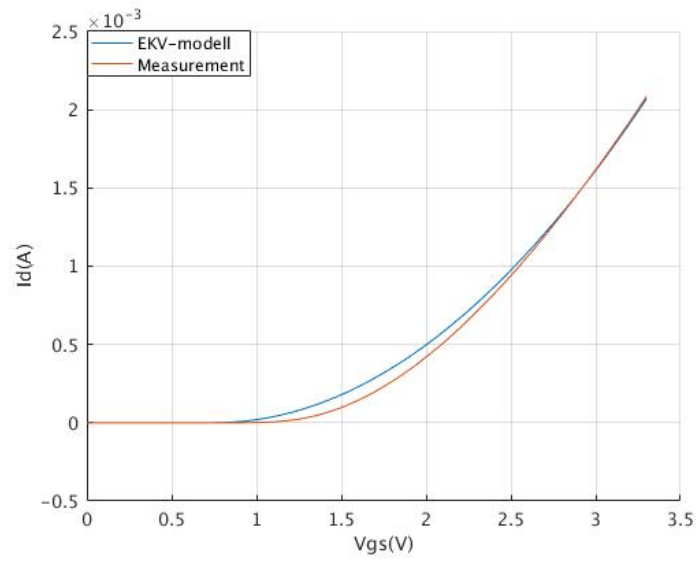


FIGURE 24. Changed values in EKV-model: $\beta_N = 100 \cdot 10^{-6}$, $V_{tn} = 0.75V$, $\lambda = 0.3$, $n = 1.25$.



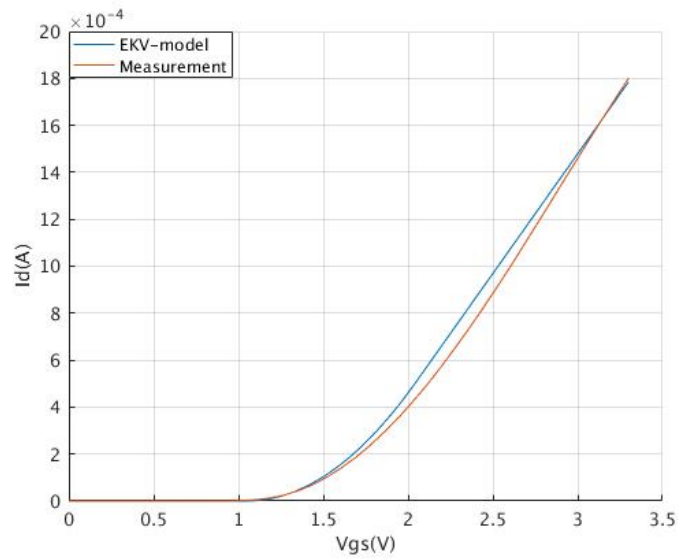


FIGURE 25. Changed values in EKV-model: $\beta_N = 204 \cdot 10^{-6}$, $V_{tn} = 1.05V$, $\lambda = 0.25$, $n = 1$.

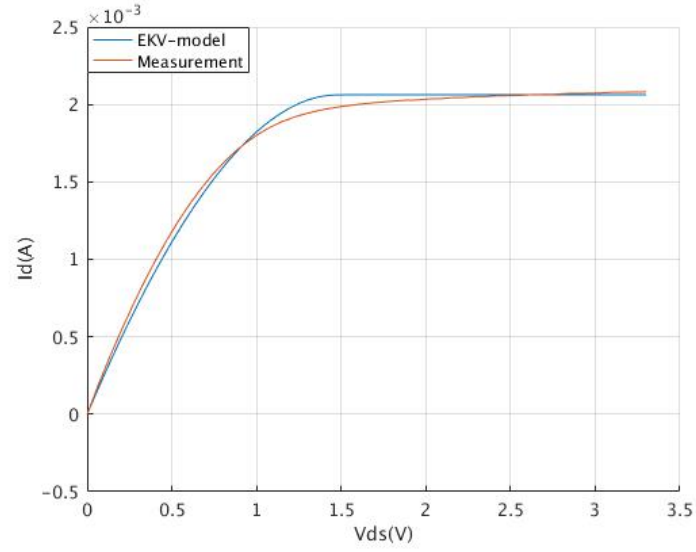

FIGUR 26. Changed values in EKV-model: $\beta_N = 290 \cdot 10^{-6}$, $V_{tn} = 0.9V$, $\lambda = 0.1$, $n = 1.62$.

6. TASK 6

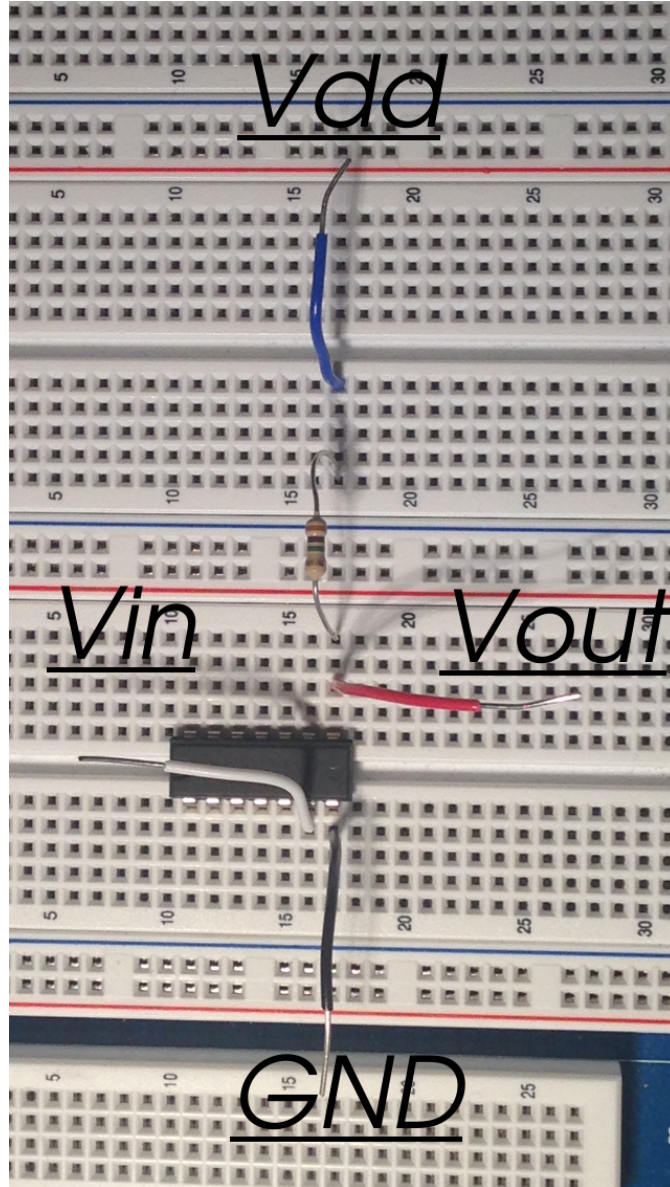

FIGUR 27. Elvis board setup for task 6.

```

1 clear all;
2 addpath(genpath('/hom/mes/src/matlab/gpib/linux'));
3 HPE3631_Init;
4 K617_Init;
5 K617_SetMode('V');
6
7 %Setter Vdd = 4
8 Vdd=4;
9 HPE3631_SetVolt(2,Vdd);
10
11 %Setter antall ganger vi måler Vout
12 count = 40;
13 Vgs=linspace(0,Vdd,count);
14
15 for i=1: length(Vgs)
16     HPE3631_SetVolt(1,Vgs(i));
17     pause(0.1);
18     Vout(i)= K617_ReadQuick;
19
20
21 end
22 HPE3631_SetVolt (1, 0);
23 HPE3631_SetVolt (2, 0);
24 HPE3631_SetVolt (3, 0);
25
26
27 figure(1);
28 plot(Vgs,Vout);
29 xlabel('Vgs(V)');
30 ylabel('Vout(V)');
31 grid on;

```

Matlab code used in task 6.


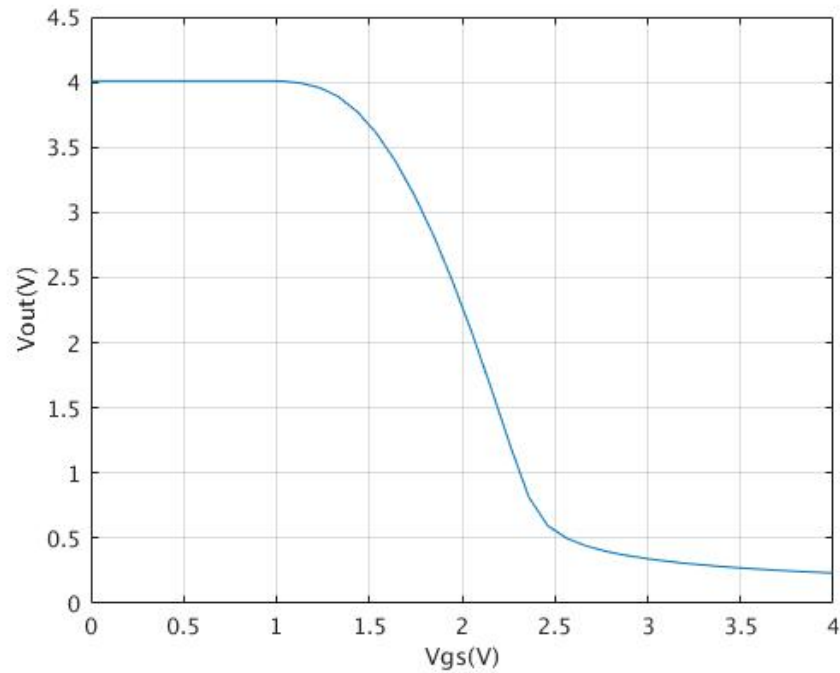


FIGURE 28. $R_D = 4,7k\Omega$. For this common source amp a V_{GS} that would bias the linear range nicely would be around 2V. The bias current at this point can be calculated using Ohm's law, $U = R * I \Rightarrow I = U/R \Rightarrow I_D = (V_{dd} - V_{out})/R_D \Rightarrow I_D = (4V - 2V)/4,7k\Omega = 0,42553mA$.

We found the gain of the common source amp to be -3,76.

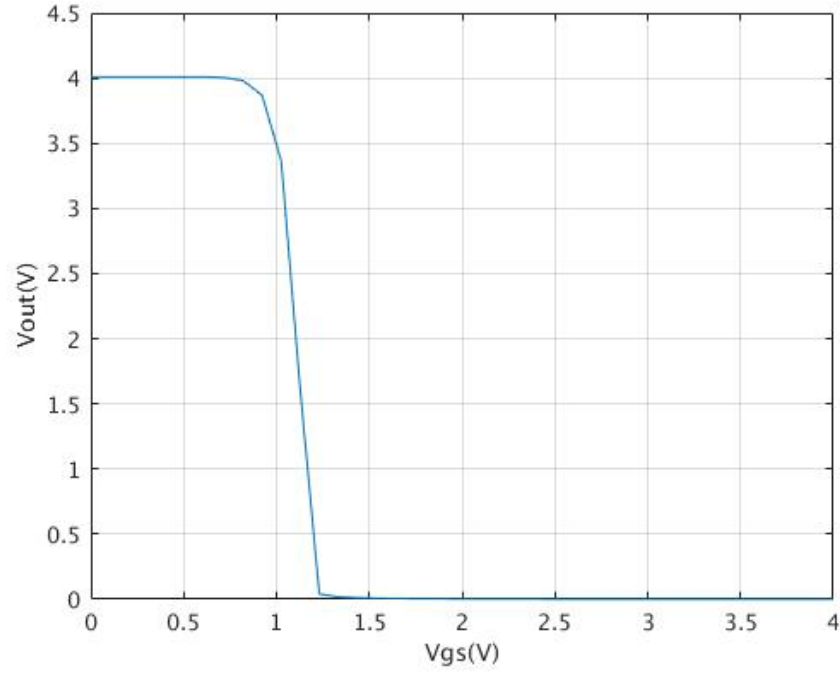We can see that the common source amp is not in weak inversion. We assume that V_{tn} isn't bigger than 0,6V (couldn't find a threshold voltage in the datasheet for the MC14007UB) and the curve doesn't start falling before $V_{gs} = 1,1V$.






FIGUR 29. $R_D = 680k\Omega$. For this common source amp a V_{GS} that would bias the linear range nicely would be around 1,13V. The bias current at this point can be calculated using Ohm's law. $I_D = (4V - 1,13V)/680k\Omega = 0,00422mA$

We found the gain of the common source amp to be -16,19.

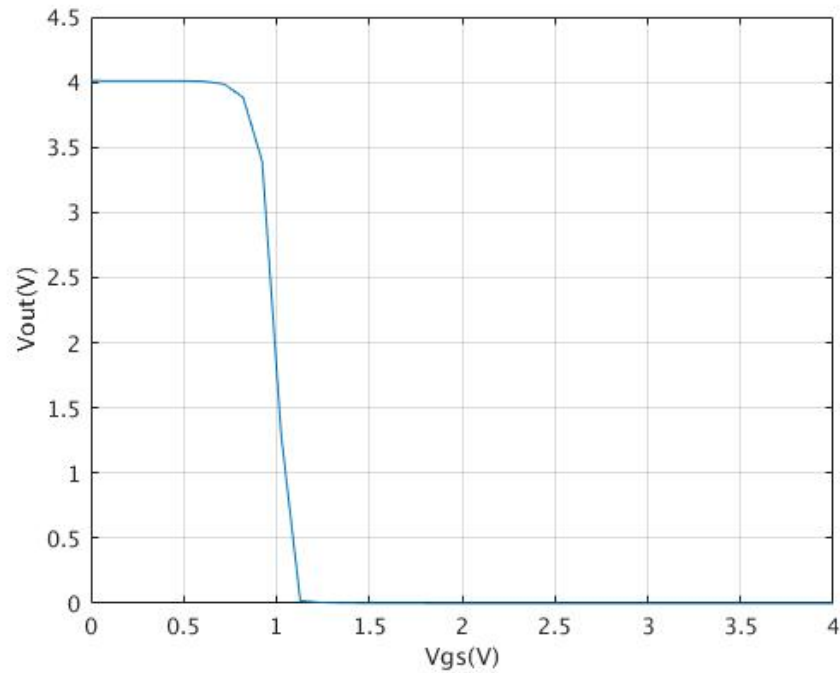Using the same assumptions as in the last plot. We see that we're still not in weak inversion.



FIGUR 30. $R_D = 3M\Omega$. For this common source amp a V_{GS} that would bias the linear range nicely would be around 1,025V. The bias current at this point can be calculated using Ohm's law. $I_D = (4V - 1,025V)/3M\Omega = 0,00099mA$

We found the gain of the common source amp to be -20,37.

Using the same assumptions as in the first plot. We can now see that we're close to the threshold, but we're still in strong inversion.

We observe that when R_D has a higher resistance, the gain increases and the bandwidth decreases. The common source amplifier with $R_D = 3M\Omega$ has the biggest gain, and the common source amp with $R_D = 4,7k\Omega$ has the highest bandwidth.