

Electrical noise – counter measures and calculation

Mandatory task 1

Rikesh Chauhan

`rikesh.chauhan@fys.uio.no`

1 LM741

1.1 Transient Analysis

Resistors R_{11} and R_{12} makes a negative feedback network. Inut is applied in the positive terminal, so it is a non-inverting amplifier.

Since the gain of a non-inverting amplifier is given as $A_v = 1 + R_{11}/R_{12}$, and R_{11} and R_{12} have values 10K and 1K, the gaon is 11 in theory.

Relation between DC input, AC input, gain and output range...

From figure 2 and 1, it is seen that DC-offset interval is -300 mV to 200 mV. When the offset is beyond this interval the ouput saturates to either +ve or -ve supply rail.

1.2 AC Analysis

1.3 DC-offset

1.4 Load capacitance

2 Frequency characteristics of some curves

2.1 FFT

2.2 FFT-2

2.3 Tuning

3 Decoupling capacitors

Given $L = 10 \text{ nH}$ for each capacitor, triangular wave with $V_{pp} 0-1\text{A}$, $T_r = T_f = 5\text{ns}$, $T_{on} = 0$, period = $10\mu\text{s}$, to be stable within 5% of 1.5V, lower corner frequency at 1MHz.

3.1 a

Low frequency target impedance $Z_t = k dV/dI$ where k is 2, dV is 0.075 and dI is 1A, hence 0.15 Ohm.

3.2 b

$n = 2L/Z_t t_r$, where L is 10H, t_r is 5 ns 27

3.3 c

Also X_c must be $< Z_t$ 1.1 uF which is 40nF for each.

3.4 d

3.5 f

3.6 f

4 Parasitic capacitive coupling

4.1 Noise captured

4.2 Noise after shielding

5 Artificial source of transient analysis

5.1 BV sources

5.2 BV sources-2

5.3 BV source file-1

5.4 Bv source file-2

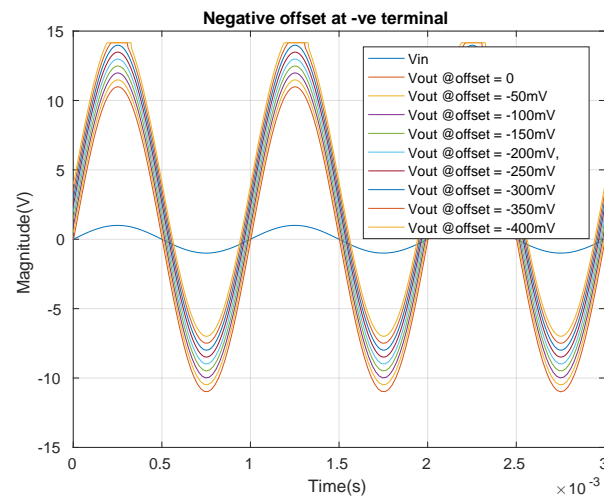


Figure 1: V_{out} with -ve offset at -ve terminal

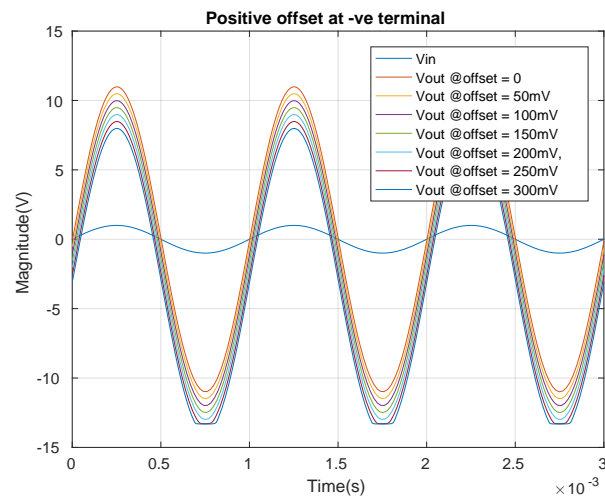


Figure 2: Vout with +ve offset at -ve terminal

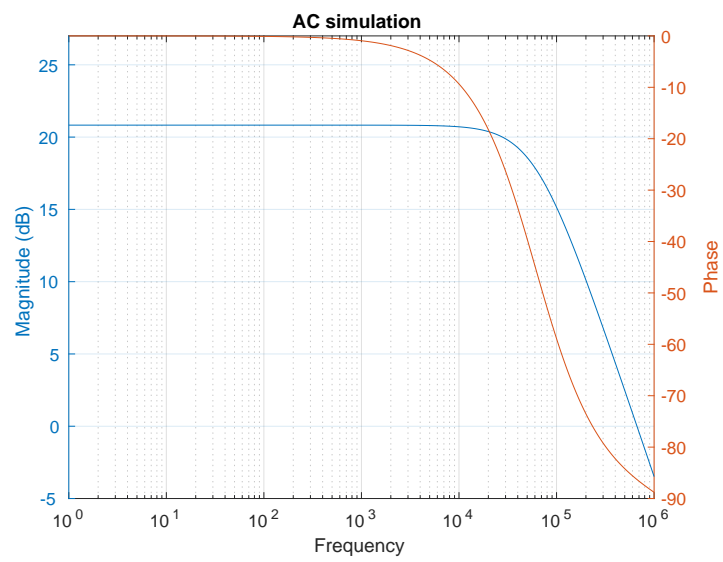


Figure 3: AC analysis of given opamp

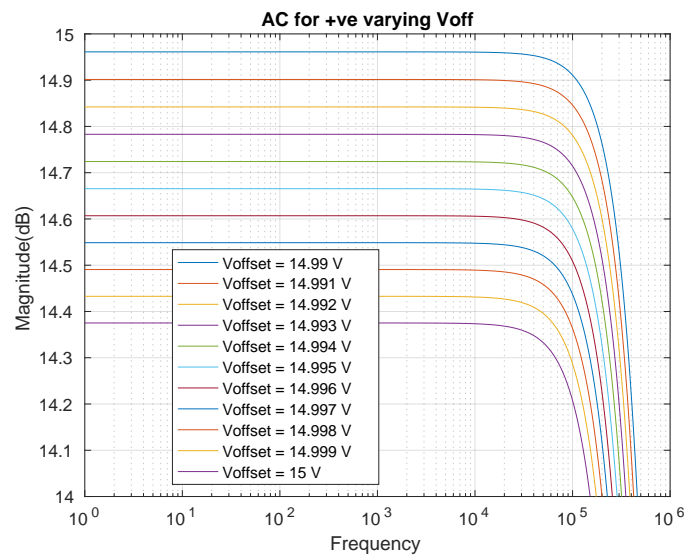


Figure 4: AC analysis with varying +ve offset

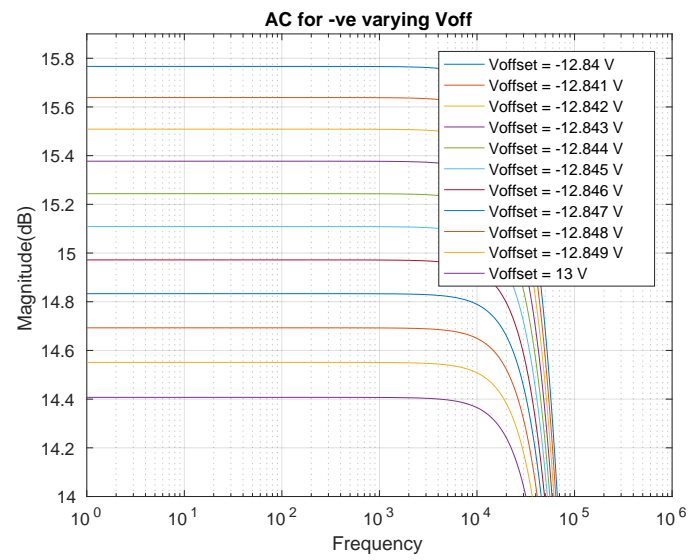


Figure 5: AC analysis with varying -ve offset

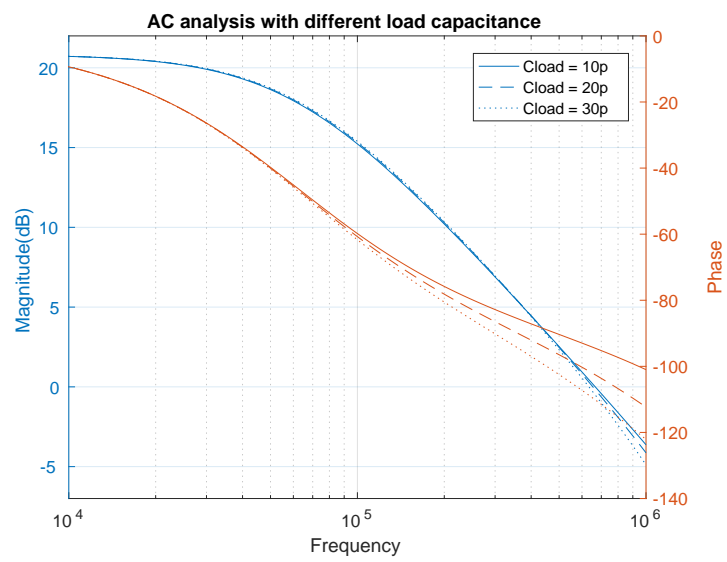


Figure 6: AC analysis with different load capacitance

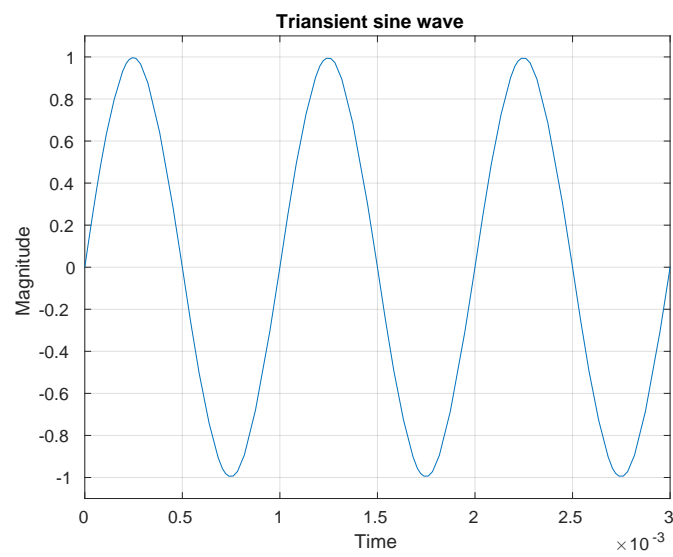


Figure 7: Sine wave

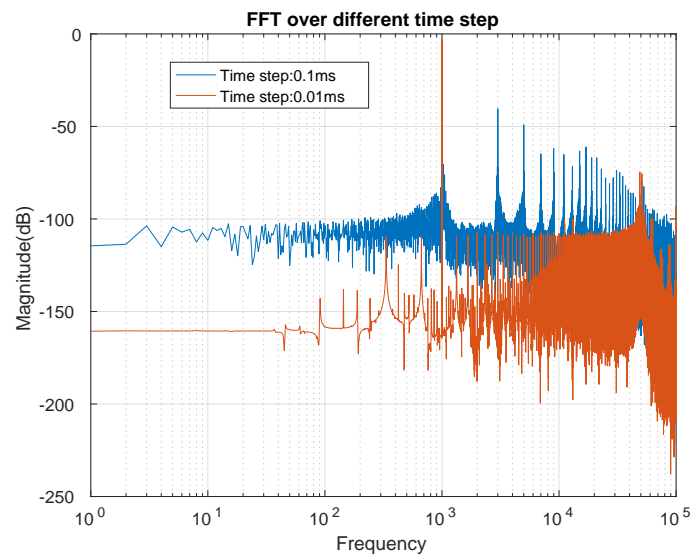


Figure 8: FFT of 7 with different time step

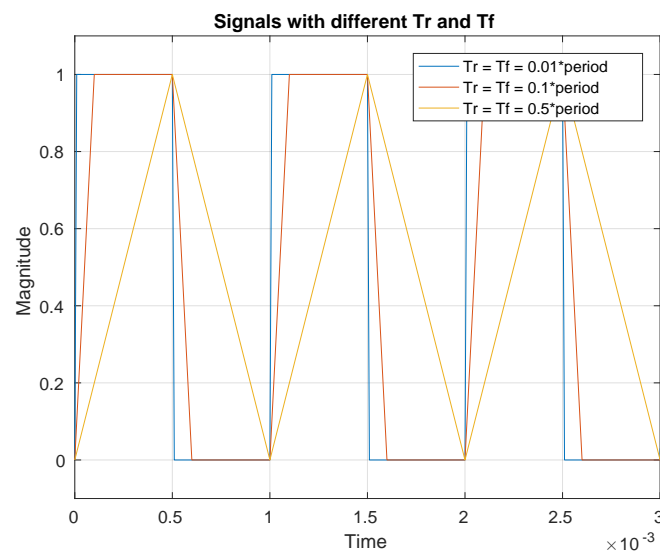


Figure 9: Signals with different rise and fall time

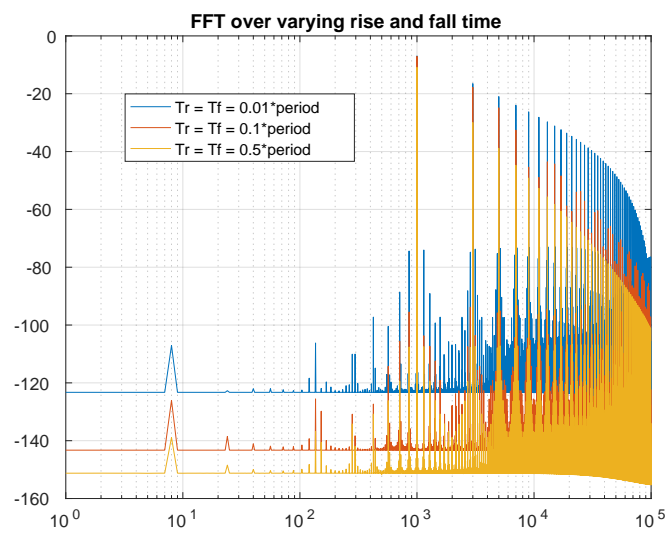


Figure 10: FFT of 9 signals

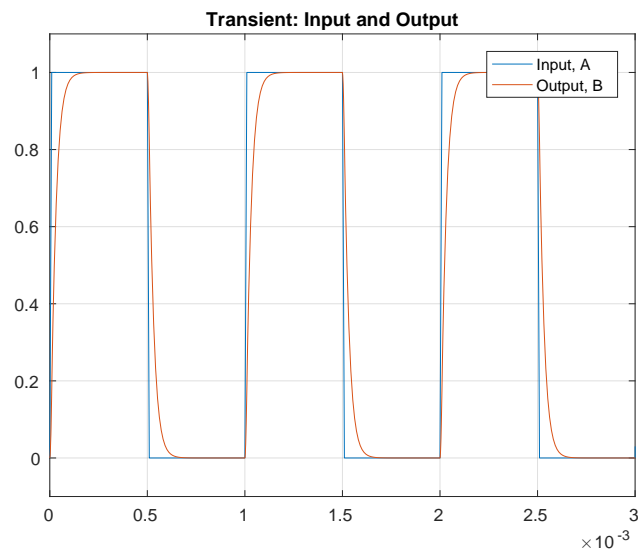


Figure 11: Input and output of LP filter

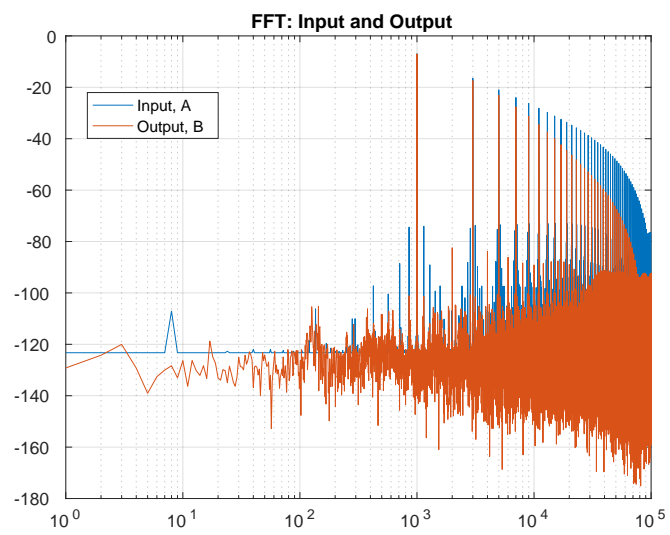


Figure 12: FFT of 11 signals